

Digital Electronics Basic Concepts

Digital Electronics

NUMBER SYSTEM

Numbers Every number system is associated with a base or radix

A positional notation is commonly used to express numbers

$$(a_5a_4a_3a_2a_1a_0)_r = a_5r^5 + a_4r^4 + a_3r^3 + a_2r^2 + a_1r^1 + a_0r^0$$

The decimal system has a base of 10 and uses symbols (0,1,2,3,4,5,6,7,8,9) to represent numbers

$$(2009)_{10} = 2 \times 10^3 + 0 \times 10^2 + 0 \times 10^1 + 9 \times 10^0$$

$$(123.24)_{10} = 1 \times 10^2 + 2 \times 10^1 + 3 \times 10^0 + 2 \times 10^{-1} + 4 \times 10^{-2}$$

An octal number system has a base 8 and uses symbols (0,1,2,3,4,5,6,7)

$$(2007)_8 = 2 \times 8^3 + 0 \times 8^2 + 0 \times 8^1 + 7 \times 8^0$$

What decimal number does it represent?

$$(2007)_8 = 2 \times 512 + 0 \times 64 + 0 \times 8^1 + 7 \times 8^0 = 1033$$

A hexadecimal system has a base of 16

Number	Symbol
0	0
1	1
2	2
3	3
4	4
5	5
6	6
7	7
8	8
9	9
10	A
11	B
12	C
13	D
14	E
15	F

$$(2BC9)_{10} = 2 \times 16^3 + B \times 16^2 + C \times 16^1 + 9 \times 16^0$$

How do we convert it into decimal number?


$$(2BC9)_{10} = 2 \times 4096 + 11 \times 256 + 12 \times 16^1 + 9 \times 16^0 = 11209$$

A Binary system has a base 2 and uses only two symbols
0, 1 to represent all the numbers

$$(1101)_2 = 1 \times 2^3 + 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0$$

Which decimal number does this correspond to ?
 
$$(1101)_2 = 1 \times 8 + 1 \times 4 + 0 \times 2^1 + 1 \times 2^0 = 13$$



2^{-1}	2^{-2}	2^{-3}	2^{-4}	2^{-5}	2^{-6}
0.5	0.25	0.125	0.0625	0.03125	0.015625

2^0	1
2^1	2
2^2	4
2^3	8
2^4	16
2^5	32
2^6	64
2^7	128
2^8	256
2^9	512
2^{10}	1024(K)
2^{20}	1048576(M)

Developing Fluency with Binary Numbers

$$1\ 1\ 0\ 0\ 1 = ? \quad 25$$

$$1100001 = ? \quad 64+32+1=97$$

$$0.101 = ? \quad 0.5+0.125=0.625$$

$$11.001 = ? \quad 3+0.125=3.125$$

Converting decimal to binary number

Convert 45 to binary number

$$(45)_{10} = b_n b_{n-1} \dots b_0$$

$$45 = b_n 2^n + b_{n-1} 2^{n-1} \dots b_1 2^1 + b_0$$

Divide both sides by 2

$$\frac{45}{2} = 22.5 = b_n 2^{n-1} + b_{n-1} 2^{n-2} \dots b_1 2^0 + b_0 \times 0.5$$

$$22 + 0.5 = b_n 2^{n-1} + b_{n-1} 2^{n-2} \dots + b_1 2^0 + b_0 \times 0.5$$

$$\Rightarrow b_0 = 1$$

$$22 + 0.5 = b_n 2^{n-1} + b_{n-1} 2^{n-2} \dots + b_1 2^0 + b_0 \times 0.5$$

$$\Rightarrow b_0 = 1$$

$$22 = b_n 2^{n-1} + b_{n-1} 2^{n-2} \dots b_2 2^1 + b_1 2^0$$

Divide both sides by 2

$$\frac{22}{2} = 11 = b_n 2^{n-2} + b_{n-1} 2^{n-3} \dots b_2 2^0 + b_1 \times 0.5$$

$$\Rightarrow b_1 = 0$$

$$11 = b_n 2^{n-2} + b_{n-1} 2^{n-3} \dots + b_3 2^1 + b_2 2^0$$

$$5.5 = b_n 2^{n-3} + b_{n-1} 2^{n-4} \dots + b_3 2^0 + 0.5b_2$$

$$\Rightarrow b_2 = 1$$

$$5 = b_n 2^{n-3} + b_{n-1} 2^{n-4} \dots b_4 2^1 + b_3 2^0$$

$$5 = b_n 2^{n-3} + b_{n-1} 2^{n-4} \dots b_4 2^1 + b_3 2^0$$

$$2.5 = b_n 2^{n-4} + b_{n-1} 2^{n-5} \dots b_4 2^0 + 0.5b_3 \Rightarrow b_3 = 1$$

$$2 = b_n 2^{n-4} + b_{n-1} 2^{n-5} \dots b_5 2^1 + b_4 2^0$$

$$1 = b_n 2^{n-5} + b_{n-1} 2^{n-6} \dots b_5 2^0 + 0.5b_4 \Rightarrow b_4 = 0$$

$$\Rightarrow b_5 = 1$$

$$(45)_{10} = b_5 b_4 b_3 b_2 b_1 b_0 = 101101$$

Converting decimal to binary number

Method of successive division by 2

45	remainder
22	1
11	0
5	1
2	1
1	0
0	1

45 = 1 0 1 1 0 1

The diagram illustrates the conversion of the decimal number 45 to its binary equivalent, 101101, using the method of successive division by 2. A table shows the sequence of divisions and their remainders. Red arrows indicate that the remainders are read from bottom to top to form the binary number. The final result is shown as 45 = 1 0 1 1 0 1.

Convert $(153)_{10}$ to octal number system

$$(153)_{10} = (b_n b_{n-1} \dots b_0)_8$$

$$(153)_{10} = b_n 8^n + b_{n-1} 8^{n-1} \dots b_1 8^1 + b_0$$

Divide both sides by 8

$$\frac{153}{8} = 19.125 = b_n 8^{n-1} + b_{n-1} 8^{n-2} \dots b_1 8^0 + \frac{b_0}{8} \Rightarrow \frac{b_0}{8} = 0.125 \Rightarrow b_0 = 1$$

153	remainder
19	1
2	3
0	2

$$153 = (231)_8$$

Converting decimal to binary number

Convert $(0.35)_{10}$ to binary number

$$(0.35)_{10} = 0.b_{-1}b_{-2}b_{-3}\dots\dots b_{-n}$$

$$0.35 = 0 + b_{-1}2^{-1} + b_{-2}2^{-2} + \dots\dots b_{-n}2^{-n}$$

How do we find the b_{-1} b_{-2} ...coefficients?

Multiply both sides by 2

$$0.7 = b_{-1} + b_{-2}2^{-1} + \dots\dots b_{-n}2^{-n+1}$$

$$\Rightarrow b_{-1} = 0$$

$$0.7 = b_{-2}2^{-1} + b_{-3}2^{-2} + \dots\dots b_{-n}2^{-n+1}$$

$$0.7 = b_{-2}2^{-1} + b_{-3}2^{-2} + \dots b_{-n}2^{-n+1}$$

Multiply both sides by 2

$$1.4 = b_{-2} + b_{-3}2^{-1} + \dots b_{-n}2^{-n+2}$$

Note that $\frac{1}{2} + \frac{1}{4} + \frac{1}{8} + \dots \leq 1$ $\Rightarrow b_{-2} = 1$

$$0.4 = b_{-3}2^{-1} + b_{-4}2^{-2} \dots b_{-n}2^{-n+2}$$

$$0.8 = b_{-3} + b_{-4}2^{-1} \dots b_{-n}2^{-n+3} \Rightarrow b_{-3} = 0$$

Converting decimal to binary number

$$0.125 = ?$$

	0 .	125	
			x2
	0 .	25	
			x2
	0 .	5	
			x2
0.125 = (.001) ₂	1 .	0	

$$0.8125 = ?$$

	0 .	8125	
			x2
	1 .	625	
			x2
	1 .	25	
			x2
0.8125 = (.1101) ₂	0 .	5	
	1 .	0	

Binary numbers

Most significant bit or **MSB**

Least significant bit or **LSB**

1011000111

This is a 10 bit number

Binary digit = bit

decimal	2bit	3bit	4bit	5bit
0	00	000	0000	00000
1	01	001	0001	00001
2	10	010	0010	00010
3	11	011	0011	00011
4		100	0100	00100
5		101	0101	00101
6		110	0110	00110
7		111	0111	00111
8			1000	01000
9			1001	01001
10			1010	01010
11			1011	01011
12			1100	01100
13			1101	01101
14			1110	01110
15			1111	01111


N-bit binary number can represent numbers from 0 to $2^N - 1$

Converting Binary to Hex and Hex to Binary


$$(b_7 b_6 b_5 b_4 b_3 b_2 b_1 b_0)_b = (h_1, h_0)_{Hex}$$

$$b_7 2^7 + b_6 2^6 + b_5 2^5 + b_4 2^4 + b_3 2^3 + b_2 2^2 b_1 2^1 + b_0 = h_1 16^1 + h_0$$
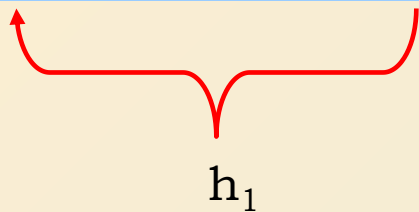
$$(b_7 2^3 + b_6 2^2 + b_5 2^1 + b_4) 2^4 + (b_3 2^3 + b_2 2^2 b_1 2^1 + b_0) = h_1 16^1 + h_0$$



$$h_1$$

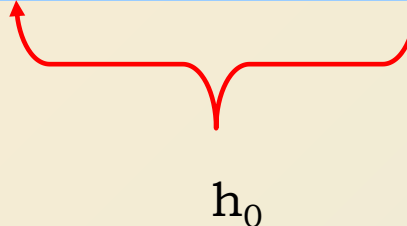

$$h_0$$

$$(10110011)_b = (1011)(0011) = (B3)_{Hex}$$

$$(110011)_b = (11)(0011) = (33)_{Hex}$$

$$(EC)_{Hex} = (1110)(1100) = (11101100)_b$$


Number	Symbol
0(0000)	0
1(0001)	1
2(0010)	2
3(0011)	3
4(0100)	4
5(0101)	5
6(0110)	6
7(0111)	7
8(1000)	8
9(1001)	9
10(1010)	A
11(1011)	B
12(1100)	C
13(1101)	D
14(1110)	E
15(1111)	F

Binary Addition/Subtraction

0	1	0	1	1
<u>0</u>	<u>0</u>	<u>1</u>	<u>1</u>	<u>1</u>
<u>0</u>	<u>1</u>	<u>1</u>	<u>1 0</u>	<u>1 1</u>

1 0 1	1 1 0 1
<u>1 1 0</u>	<u>+ 1 1 1 0</u>
<u>1 0 1 1</u>	<u>1 1 0 1 1</u>

Complement of a number

 

9's complement of n-digit number x is $10^n - 1 - x$

10's complement of n-digit number x is $10^n - x$

9's complement of 85 ?


$$10^2 - 1 - 85$$

$$99 - 85 = 14$$

$$9's \text{ complement of } 123 = 999 - 123 = 876$$

$$10's \text{ complement of } 123 = 9's \text{ complement of } 123 + 1 = 877$$

Complement of a binary number

 

1's complement of n-bit number x is $2^n - 1 - x$

2's complement of n-bit number x is $2^n - x$

1's complement of 1011 ?

$$2^4 - 1 - 1011$$

$$1111 - 1011 = 0100$$

1's complement is simply obtained by flipping a bit (changing 1 to 0 and 0 to 1)

1's complement of 1001101 = ?

0110010

2's complement of 1010 = 1's complement of 1010 + 1 = 0110

2's complement of 110010 =


Leave all least significant 0's as they are, leave first 1 unchanged and then flip all subsequent bits

001110


1011 → 0101

101101100 → 010010100

Advantages of using 2's complement

 


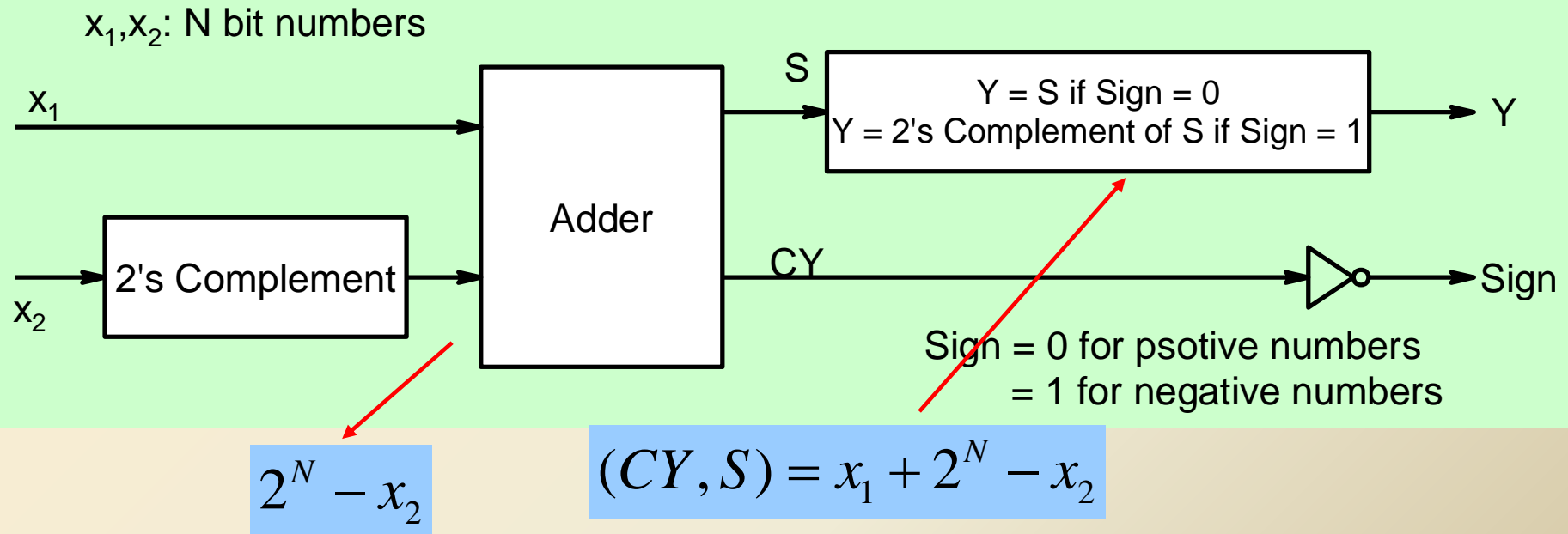Can we carry out $Y = X_1 - X_2$ using such an adder?



Note that carry will be there only if $x_1 - x_2$ is positive as 2^N is $N+1$ bits (1 followed by N zeros)

Advantages of using 2's complement

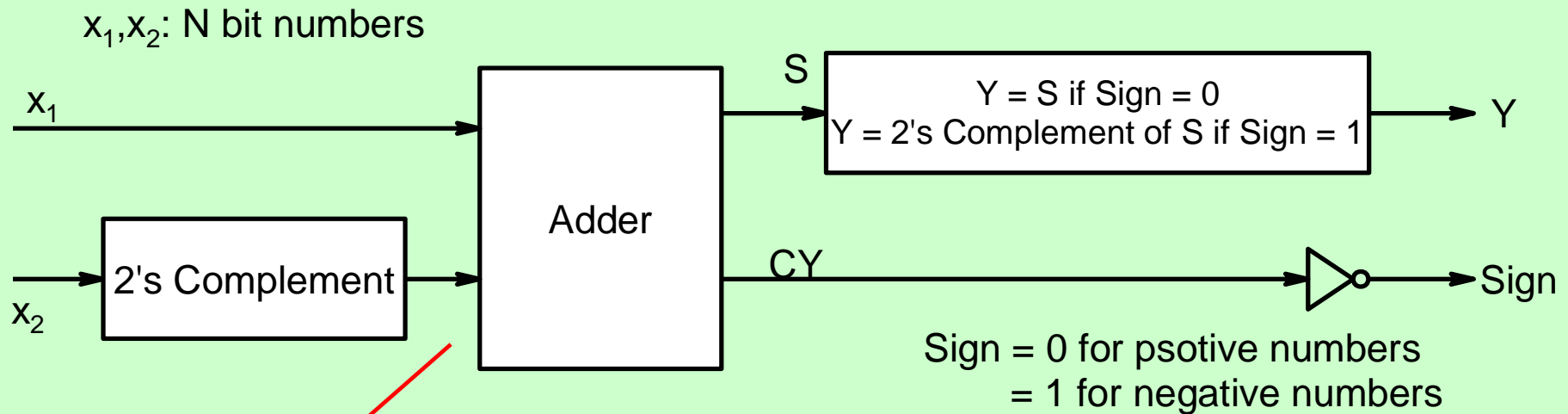

$$2^N - x_2$$

$$(CY, S) = x_1 + 2^N - x_2$$


Note that carry will be there only if $x_1 - x_2$ is positive as 2^N is N+1 bits (1 followed by N zeros)

A zero carry implies a negative number whose magnitude ($x_2 - x_1$) can be found as follows:

$$S = x_1 + 2^N - x_2$$


$$\text{2's complement of } S = 2^N - (x_1 + 2^N - x_2) = x_2 - x_1$$

Example

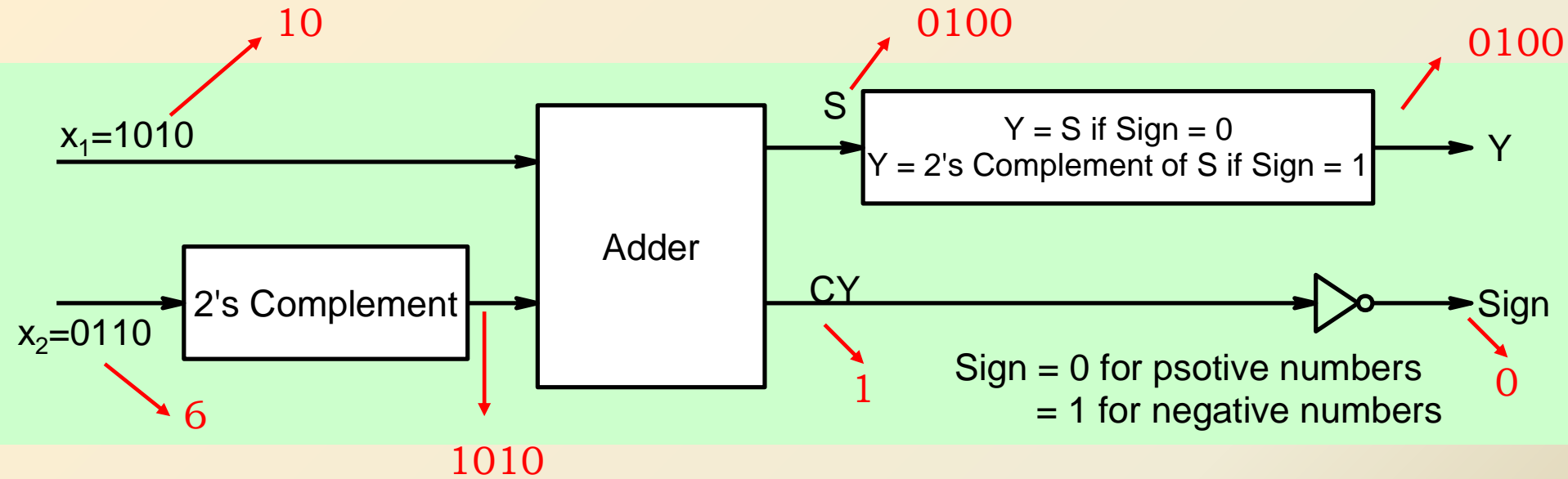

$$\begin{array}{r} 1010 \\ + 1010 \\ \hline 10100 \end{array}$$


Example

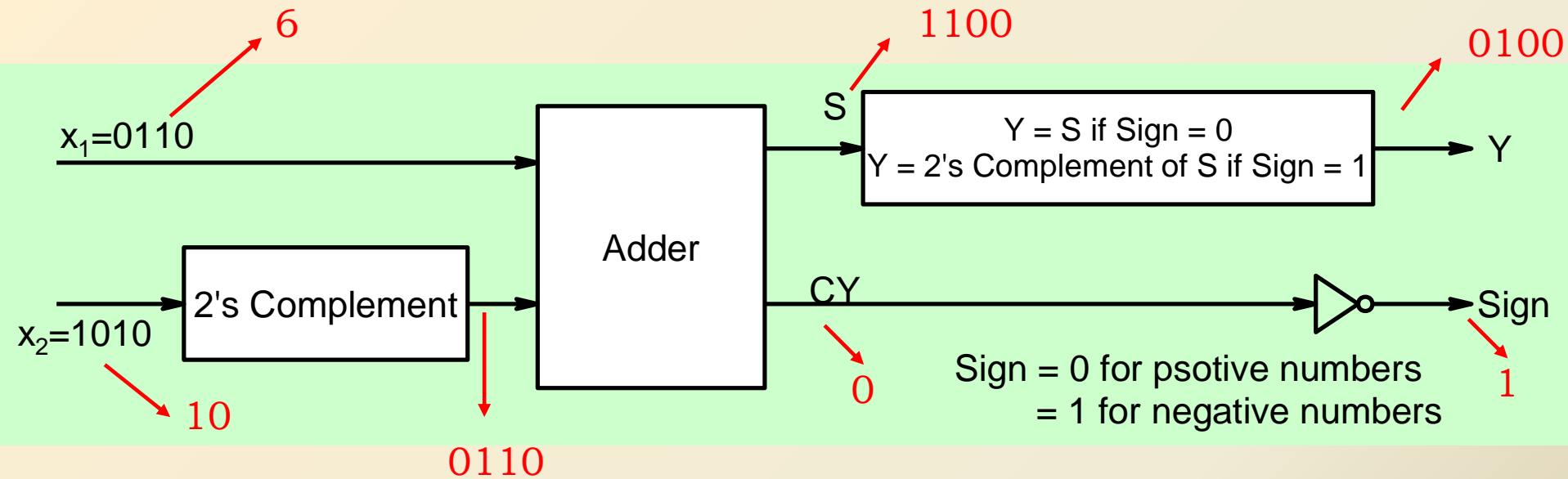

$$\begin{array}{r} 0110 \\ + 0110 \\ \hline 1100 \end{array}$$

It makes sense to use adder as a subtractor as well provided additional circuit required for carrying out 2's complement is simple

Subtraction using 10's complement

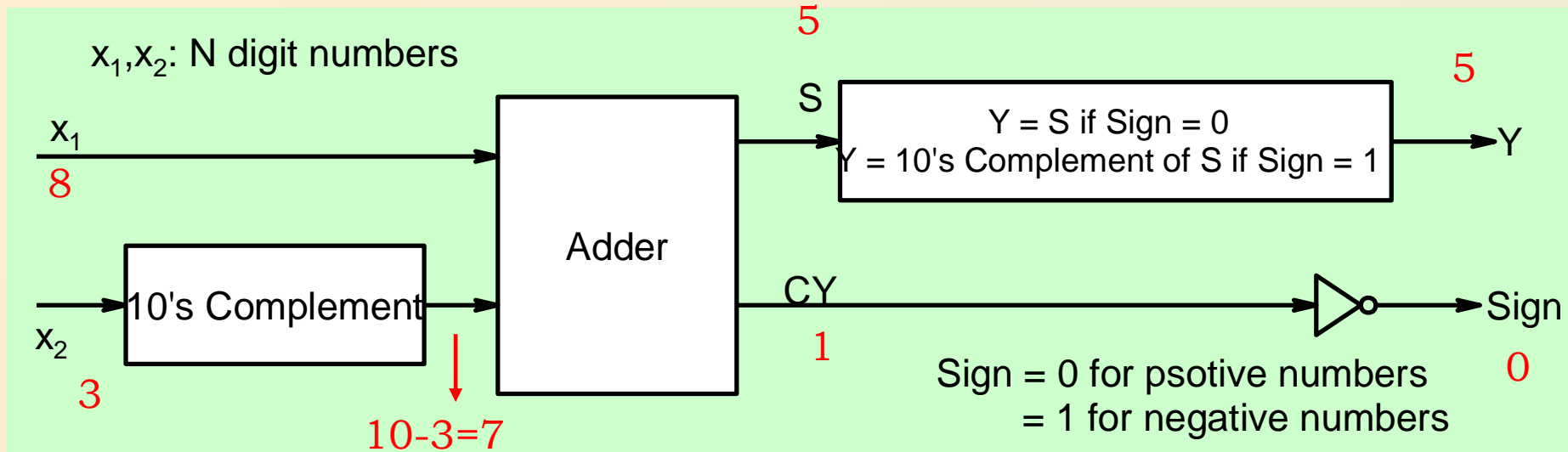

This way of subtraction would make sense only if subtracting a number x_2 from 10^N is much simpler than directly subtracting it directly from x_1

Representing positive and negative binary numbers

One extra bit is required to carry sign information. Sign bit = 0

Represents positive number and Sign bit = 1 represents negative number



decimal	Signed Magnitude
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
-0	1000
-1	1001
-2	1010
-3	1011
-4	1100
-5	1101
-6	1110
-7	1111

decimal	Signed 1's complement
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
-0	1111
-1	1110
-2	1101
-3	1100
-4	1011
-5	1010
-6	1001
-7	1000


Internshala Trainings

decimal	Signed 2's complement
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
-1	1111
-2	1110
-3	1101
-4	1100
-5	1011
-6	1010
-7	1001

 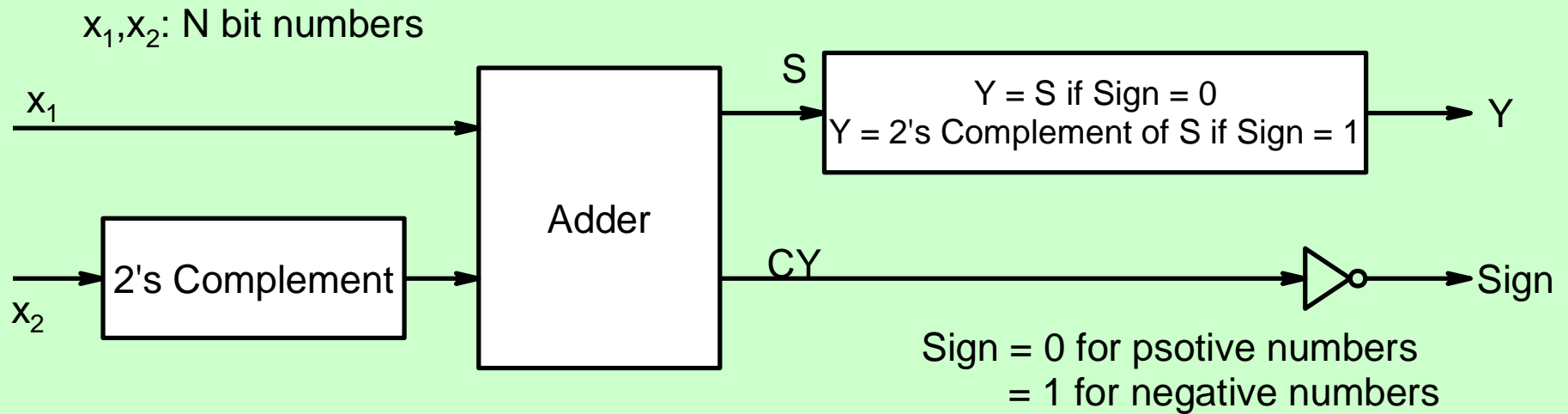If we represent numbers in 2's complement form carrying out subtraction is same as addition



Example

 

$$\begin{array}{r} + 5 \\ + 2 \\ \hline + 7 \\ \hline \end{array}$$

$$\begin{array}{r} 0101 \\ + 0010 \\ \hline 0111 \\ \hline \end{array}$$

$$\begin{array}{r} + 5 \\ - 2 \\ \hline + 3 \\ \hline \end{array}$$

$$\begin{array}{r} 0101 \\ + 1110 \\ \hline 0011 \\ \hline \end{array}$$

$$\begin{array}{r} - 5 \\ + 2 \\ \hline - 3 \\ \hline \end{array}$$

$$\begin{array}{r} 1011 \\ + 0010 \\ \hline 1101 \\ \hline \end{array}$$

$$\begin{array}{r} - 5 \\ - 2 \\ \hline - 7 \\ \hline \end{array}$$

$$\begin{array}{r} 1011 \\ + 1110 \\ \hline 1001 \\ \hline \end{array}$$

2's complement is 0011 = 3

Internshala Trainings


2's complement is 0111 = 7

BOOLEAN ALGEBRA

Boolean Algebra


Algebra on Binary numbers

 A variable x can take two values $\{0,1\}$



Basic operations:

AND: $y = x_1 \cdot x_2$

 

Y is 1 if and only if both x_1 and x_2 are 1, otherwise zero

Truth Table

x_1	x_2	y
0	0	0
0	1	0
1	0	0
1	1	1

Basic operations:

$$\text{OR: } y = x_1 + x_2$$

Y is 1 if either x_1 and x_2 is 1. Or $y = 0$ if and only if both variables are zero

x_1	x_2	y
0	0	0
0	1	1
1	0	1
1	1	1

$$\text{NOT: } y = \bar{x}$$

x	y
0	1
1	0

Boolean Algebra

Basic Postulates

$$P1: \quad x + 0 = x$$

$$P2: \quad x + y = y + x$$

$$P3: \quad x.(y+z) = x.y+x.z$$

$$P4: \quad x + \bar{x} = 1$$

$$P1: \quad x . 1 = x$$

$$P2: \quad x . y = y . x$$

$$P3: \quad x+y.z = (x+y).(x+z)$$

$$P4: \quad x . \bar{x} = 0$$

Basic Theorems

$$T1: \quad x + x = x$$

$$T2: \quad x + 1 = 1$$

$$T3: \quad \overline{\bar{x}} = x$$

$$T4: \quad x + (y+z) = (x+y)+z$$

$$T5: \quad \overline{(x+y)} = \bar{x} . \bar{y} \text{ (DeMorgan's theorem)}$$

$$T6: \quad x + x.y = x$$

$$T1: \quad x . x = x$$

$$T2: \quad x . 0 = 0$$

$$T4: \quad x . (y.z) = (x.y).z$$

$$T5: \quad \overline{(x.y)} = \bar{x} + \bar{y} \text{ (DeMorgan's theorem)}$$

$$T6: \quad x.(x+y) = x$$

Proving theorems

$$\text{P1: } x + 0 = x$$

$$\text{P2: } x + y = y + x$$

$$\text{P3: } x.(y+z) = x.y+x.z$$

$$\text{P4: } x + \bar{x} = 1$$

$$\text{Prove T1: } x + x = x$$

$$x + x = (x+x). 1 \text{ (P1)}$$

$$= (x+x). (\overline{x+x}) \text{ (P4)}$$

$$= x + x.\bar{x} \text{ (P3)}$$

$$= x + 0 \text{ (P4)}$$

$$= x \text{ (P1)}$$

$$\text{P1: } x . 1 = x$$

$$\text{P2: } x . y = y . x$$

$$\text{P3: } x+y.z = (x+y).(x+z)$$

$$\text{P4: } x . \bar{x} = 0$$

$$\text{Prove T1: } x . x = x$$

$$x . x = x.x+ 0 \text{ (P1)}$$

$$= x.x + x.\bar{x} \text{ (P4)}$$

$$= x . (\overline{x+x}) \text{ (P3)}$$

$$= x . 1 \text{ (P4)}$$

$$= x \text{ (P1)}$$

Proving theorems

$$P1: x + 0 = x$$

$$P2: x + y = y + x$$

$$P3: x.(y+z) = x.y+x.z$$

$$P4: x + \bar{x} = 1$$

$$P1: x . 1 = x$$

$$P2: x . y = y . x$$

$$P3: x+y.z = (x+y).(x+z)$$

$$P4: x . \bar{x} = 0$$

$$\text{Prove : } x + 1 = 1$$

$$x + 1 = x + (x + \bar{x})$$

$$= (x+x) + \bar{x}$$

$$= x + \bar{x}$$

$$= 1$$

$$\begin{aligned} x + x . y &= x \\ &= x . 1 + x . y \\ &= x . (1 + y) \\ &= x . 1 \\ &= x \end{aligned}$$

$$\begin{aligned} x + \bar{x} . y &= x + y \\ &= (x + \bar{x}) . (x + y) \\ &= 1 . (x + y) \\ &= x + y \end{aligned}$$

DeMorgan's theorem

$$\overline{(x_1 + x_2 + x_3 + \dots)} = \bar{x}_1 . \bar{x}_2 . \bar{x}_3 .$$

$$\overline{(x_1 . x_2 . x_3 \dots)} = (\bar{x}_1 + \bar{x}_2 + \bar{x}_3 + \dots)$$

Simplification of Boolean expressions

$$\overline{(\overline{X_1} \cdot X_2 + \overline{X_2} \cdot X_3)} = ?$$



$$\overline{(X_1 + X_2 + X_3 + \dots)} = \overline{X_1} \cdot \overline{X_2} \cdot \overline{X_3} \cdot$$

$$\overline{(X_1 \cdot X_2 \cdot X_3 \dots)} = (\overline{X_1} + \overline{X_2} + \overline{X_3} + \dots)$$

$$= (X_1 + \overline{X_2}) \cdot (X_2 + \overline{X_3})$$

$$= X_1 \cdot X_2 + X_1 \cdot \overline{X_3} + \overline{X_2} \cdot \overline{X_3}$$

Function of Boolean variables

  

$$y = x^2$$

x_1	x_2	y
0	0	0
0	1	1
1	0	0
1	1	0

$Y = 1$ when x_1 is 0 and x_2 is 1

$$y = \overline{x_1} \cdot x_2$$

Boolean expression

Obtaining Boolean expressions from truth Table

x_1	x_2	y
0	0	1
0	1	0
1	0	0
1	1	0

$$y = \overline{x_1} \cdot \overline{x_2}$$

x_1	x_2	y
0	0	0
0	1	0
1	0	1
1	1	0

$$y = x_1 \cdot \overline{x_2}$$

x_1	x_2	y
0	0	1
0	1	0
1	0	0
1	1	1

$$\overline{x_1} \cdot \overline{x_2}$$

$$x_1 \cdot x_2$$

$$y = \overline{x_1} \cdot \overline{x_2} + x_1 \cdot x_2$$

Obtaining Boolean expressions from truth Table

x_1	x_2	y
0	0	0
0	1	1
1	0	1
1	1	0

$$y = \overline{x_1} \cdot x_2 + x_1 \cdot \overline{x_2}$$

Instead of writing expressions as sum of terms that make y equal to 1, we can also write expressions using terms that make y equal to 0

x_1	x_2	y
0	0	1
0	1	1
1	0	1
1	1	0

$$y = \overline{x_1} \cdot \overline{x_2} + \overline{x_1} \cdot x_2 + x_1 \cdot \overline{x_2}$$

$$y = \overline{x_1} + \overline{x_2}$$

x_1	x_2	y
0	0	1
0	1	0
1	0	1
1	1	1

$$y = x_1 + \overline{x_2}$$

x_1	x_2	y
0	0	0
0	1	1
1	0	1
1	1	1

$$y = x_1 + x_2$$

x_1	x_2	y
0	0	0
0	1	1
1	0	1
1	1	0

$$x_1 + x_2$$

$$y = (x_1 + x_2) \cdot (\overline{x_1} + \overline{x_2})$$

$$\overline{x_1} + \overline{x_2}$$

Obtaining Boolean expressions from truth Table

x_1	x_2	x_3	y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

$$y = \overline{x_1} \cdot \overline{x_2} \cdot x_3 + \overline{x_1} \cdot x_2 \cdot x_3 + x_1 \cdot \overline{x_2} \cdot x_3 + x_1 \cdot x_2 \cdot x_3$$

Sum of Products (SOP) form

$$y = (x_1 + x_2 + x_3) \cdot (x_1 + \overline{x_2} + x_3) \cdot (\overline{x_1} + x_2 + x_3) \cdot (\overline{x_1} + \overline{x_2} + x_3)$$


Product of Sum (POS) form

IMPLEMENTATION OF BOOLEAN EXPRESSIONS



Implementing Boolean expressions

Elementary Gates


$$\text{AND: } y = x_1 \cdot x_2$$

 

Why call it a gate?

  


$$\text{OR: } y = x_1 + x_2$$

 



$$\text{NOT: } y = \bar{x}$$



NAND: $y = \overline{x_1 \cdot x_2}$

 



NOR: $y = \overline{x_1 + x_2}$

  

XOR: $y = x_1 \oplus x_2 = x_1 \cdot \overline{x_2} + \overline{x_1} \cdot x_2$


x_1	x_2	y
0	0	0
0	1	1
1	0	1
1	1	0

  Y is 1 if only one variable is 1 and the other is zero



XNOR: $y = x_1 \boxdot x_2 = x_1 \cdot x_2 + \overline{x_1} \cdot \overline{x_2}$

 
Y is 1 if only both variables are either 0 or 1




$$y = x_1 \boxdot x_2 = \overline{x_1 \oplus x_2}$$

Gates with more than 2 inputs

AND: $y = x_1 \cdot x_2 \cdot x_3 \dots$

 


OR: $y = x_1 + x_2 + x_3 + \dots$

 

XOR: $y = x_1 \oplus x_2 \oplus x_3 = x_1 \cdot \overline{x_2} \cdot \overline{x_3} + \overline{x_1} \cdot x_2 \cdot \overline{x_3} + \overline{x_1} \cdot \overline{x_2} \cdot x_3 + x_1 \cdot x_2 \cdot x_3$



$Y = 1$ only if odd number of inputs is 1

 Implementing Boolean expressions using gates



$$S = \bar{x}.\bar{y}.z + \bar{x}.y.\bar{z} + x.\bar{y}.\bar{z} + x.y.z$$


$$C = x.y + x.z + y.z$$

  

Implementing gates using Switches

Voltage controlled Switch


SN:

 

Switch is closed if voltage x is HIGH
Switch is open if voltage x is LOW


Voltage controlled Switch

SP:

 


Switch is closed if voltage x is LOW
Switch is open if voltage x is HIGH

 
We have seen earlier (in class 12) that transistors act as switches !



 Switch is closed if voltage x is HIGH
Switch is open if voltage x is LOW



 
Switch is closed if voltage x is LOW
Switch is open if voltage x is HIGH



NOT gate

NAND Gate

 
$$\text{NAND: } y = \overline{x_1 \cdot x_2}$$



x_1	x_2	y
LOW	LOW	HIGH
LOW	HIGH	HIGH
HIGH	LOW	HIGH
HIGH	HIGH	LOW



NOR Gate
 
$$\text{NOR: } y = \overline{x_1 + x_2}$$




x_1	x_2	y
LOW	LOW	HIGH
LOW	HIGH	LOW
HIGH	LOW	LOW
HIGH	HIGH	LOW

Design Overview

 
 


a	b	c	S	CY
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 
$$S = \bar{x}.\bar{y}.z + \bar{x}.y.\bar{z} + x.\bar{y}.\bar{z} + x.y.z$$



$$C = x.y + x.z + y.z$$

  

Internshala Trainings

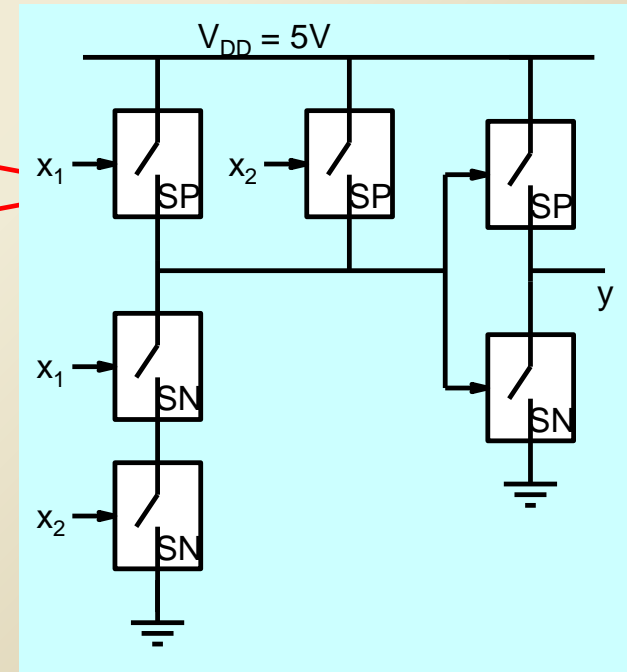

SOP AND POS REPRESENTATIONS

Representation of Boolean Expressions

x	y	f_1
0	0	0
0	1	1
1	0	1
1	1	0

x	y	min term
0	0	$\bar{x} \cdot \bar{y}$ m0
0	1	$\bar{x} \cdot y$ m1
1	0	$x \cdot \bar{y}$ m2
1	1	$x \cdot y$ m3

$$f_1 = \bar{x} \cdot y + x \cdot \bar{y}$$

$$f_1 = m_1 + m_2$$

$$f_1 = \sum (1, 2)$$

$$f_2 = \sum (0, 2, 3) = ?$$

$$f_2 = \bar{x} \cdot \bar{y} + x \cdot \bar{y} + x \cdot y$$

A minterm is a product that contains all the variables used in a function

Three variable functions

x	y	z	min terms	
0	0	0	$\bar{x} . \bar{y} . \bar{z}$	m0
0	0	1	$\bar{x} . \bar{y} . z$	m1
0	1	0	$\bar{x} . y . \bar{z}$	m2
0	1	1	$\bar{x} . y . z$	m3
1	0	0	$x . \bar{y} . \bar{z}$	m4
1	0	1	$x . \bar{y} . z$	m5
1	1	0	$x . y . \bar{z}$	m6
1	1	1	$x . y . z$	m7

$$f_2 = \sum (1, 4, 7) = ?$$

$$f_2 = \bar{x} . \bar{y} . z + x . \bar{y} . \bar{z} + x . y . z$$

Product of Sum Terms Representation

x	y	f_1
0	0	0
0	1	1
1	0	1
1	1	0

x	y	Max term
0	0	$x + \underline{y}$ M0
0	1	$\underline{x} + y$ M1
1	0	$x + \underline{y}$ M2
1	1	$\underline{x} + y$ M3

$$F1 = (x+y)(x' + y') = M_0.M_3 = \prod M_0M_3$$

x	y	z	Max. terms
0	0	0	$x + y + z$ M0
0	0	1	$x + y + \bar{z}$ M1
0	1	0	$x + \bar{y} + z$ M2
0	1	1	$x + \bar{y} + \bar{z}$ M3
1	0	0	$\bar{x} + y + z$ M4
1	0	1	$\bar{x} + y + \bar{z}$ M5
1	1	0	$\bar{x} + \bar{y} + z$ M6
1	1	1	$\bar{x} + \bar{y} + \bar{z}$ M7

$$f_1 = \Pi(1, 5, 7) = ?$$


$$f_2 = (x + y + \bar{z}).(\bar{x} + y + \bar{z}).(\bar{x} + \bar{y} + \bar{z})$$

Simplification of Boolean Expressions

x_1	x_2	x_3	y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

$$y = \sum (1, 3, 5, 7)$$

 
$$y = \bar{x}_1 \cdot \bar{x}_2 \cdot x_3 + \bar{x}_1 \cdot x_2 \cdot x_3 + x_1 \cdot \bar{x}_2 \cdot x_3 + x_1 \cdot x_2 \cdot x_3$$



Simplification of Boolean expression yields : $y = x_3$!! which does not require any gates at all !

Goal of Simplification


 
$$y = \overline{x_1} \cdot \overline{x_2} \cdot x_3 + \overline{x_1} \cdot x_2 \cdot x_3 + x_1 \cdot \overline{x_2} \cdot x_3 + x_1 \cdot x_2 \cdot x_3$$



Goal of simplification is to reduce the complexity of gate circuit. This requires that we minimize the number of gates. Since number of gates depends on number of minterms, one of the goals of simplification is to **minimize the number of minterms in SOP expression**

$$y = \overline{x_1} \cdot \overline{x_2} \cdot x_3 + \overline{x_1} \cdot x_2 \cdot x_3 + x_1 \cdot \overline{x_2} \cdot x_3 + x_1 \cdot x_2 \cdot x_3$$
  
$$\Rightarrow y = \overline{x_1} \cdot x_3 + x_1 \cdot \overline{x_2} \cdot x_3 + x_1 \cdot x_2 \cdot x_3$$



This circuit is simpler not just because it uses 4 gates instead of 5 but also because circuit-2 uses one 2-input and three 3-input gates as compared to five 3-input gates used in circuit-1

Goal of Simplification

In the SOP expression:

1. Minimize number of product terms
2. Minimize number of literals in each term

Simplification \Rightarrow Minimization

Minimization

$$y = \overline{x_1} \cdot \overline{x_2} \cdot x_3 + \overline{x_1} \cdot x_2 \cdot x_3 + x_1 \cdot \overline{x_2} \cdot x_3 + x_1 \cdot x_2 \cdot x_3$$

$$y = \overline{x_1} \cdot x_3 \cdot (\overline{x_2} + x_2) + x_1 \cdot x_3 \cdot (\overline{x_2} + x_2)$$

$$y = \overline{x_1} \cdot x_3 + x_1 \cdot x_3$$

$$y = (\overline{x_1} + x_1) \cdot x_3$$

$$y = x_3$$

Principle used: $x + \overline{x} = 1$

$$f = \bar{x} \cdot \bar{y} + \bar{x} \cdot y + x \cdot \bar{y}$$

Apply the Principle: $x + \bar{x} = 1$ to simplify

$$f = \bar{x} \cdot (\bar{y} + y) + x \cdot \bar{y}$$

$$f = \bar{x} + x \cdot \bar{y}$$

How do we simplify further?

$$f = \bar{x} \cdot \bar{y} + \bar{x} \cdot y + x \cdot \bar{y} = \bar{x} \cdot \bar{y} + \bar{x} \cdot \bar{y} + \bar{x} \cdot y + x \cdot \bar{y}$$

Principle used : $x + x = x$

$$\begin{aligned} f &= \bar{x} \cdot \bar{y} + \bar{x} \cdot y + \bar{x} \cdot \bar{y} + x \cdot \bar{y} \\ &= \bar{x} \cdot (\bar{y} + y) + (\bar{x} + x) \cdot \bar{y} = \bar{x} + \bar{y} \end{aligned}$$

Simplify

$$f = \overline{x_1} \cdot \overline{x_2} \cdot \overline{x_3} \cdot x_4 + \overline{x_1} \cdot \overline{x_2} \cdot x_3 \cdot \overline{x_4} + \overline{x_1} \cdot x_2 \cdot \overline{x_3} \cdot \overline{x_4} + \overline{x_1} \cdot x_2 \cdot x_3 \cdot \overline{x_4} + \\ \overline{x_1} \cdot \overline{x_2} \cdot x_3 \cdot x_4 + \overline{x_1} \cdot x_2 \cdot \overline{x_3} \cdot x_4$$

Principle: $x + \overline{x} = 1$ and $x + x = x$

Need a systematic and simpler method for applying these two principles

Karnaugh Map (K map) is a popular technique for carrying out simplification

It represents the information in problem in such a way that the two principles become easy to apply

KARNAUGH MAPS

K-map representation of truth table

x	y	min term
0	0	$\overline{x} \cdot \overline{y}$ m0
0	1	$\overline{x} \cdot y$ m1
1	0	$x \cdot \overline{y}$ m2
1	1	$x \cdot y$ m3


	y	
	0	1
x	0	m ₀ m ₁
	1	m ₂ m ₃

x	y	f ₁
0	0	0
0	1	1
1	0	1
1	1	0



	y	
	0	1
x	0	0 1
	1	1 0

$$f_2 = \sum (0, 2, 3)$$

 

		y	
		0	1
x	0	1	0
	1	<u>1</u>	1

		y	
		0	1
x	0	1	0
	1	0	1




$$f = \bar{x}.\bar{y} + x.y$$

3-variable K-map representation

x	y	z	min terms	
0	0	0	$\bar{x} \cdot \bar{y} \cdot \bar{z}$	m0
0	0	1	$\bar{x} \cdot \bar{y} \cdot z$	m1
0	1	0	$\bar{x} \cdot y \cdot \bar{z}$	m2
0	1	1	$\bar{x} \cdot y \cdot z$	m3
1	0	0	$x \cdot \bar{y} \cdot \bar{z}$	m4
1	0	1	$x \cdot \bar{y} \cdot z$	m5
1	1	0	$x \cdot y \cdot \bar{z}$	m6
1	1	1	$x \cdot y \cdot z$	m7

		yz			
		00	01	11	10
x	0	m ₀	m ₁	m ₃	m ₂
	1	m ₄	m ₅	m ₇	m ₆

x	y	z	f
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

 


		yz			
		00	01	11	10
x	0	0	1	1	0
	1	0	1	1	0

x \ yz	00	01	11	10
0	1	0	1	0
1	0	1	1	0

$$f = \bar{x}.\bar{y}.\bar{z} + \bar{x}.y.z + x.\bar{y}.z + x.y.z$$

4-variable K-map representation

w	x	y	z	min terms
0	0	0	0	m_0
0	0	0	1	m_1
0	0	1	0	m_2
0	0	1	1	m_3
⋮	⋮	⋮	⋮	⋮
1	1	1	0	m_{14}
1	1	1	1	m_{15}

 

wx \ yz	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

wx \ yz	00	01	11	10
00	1	0	1	0
01	0	1	1	0
11	1	0	0	1
10	1	0	0	0

$$f = \overline{w}. \overline{x}. \overline{y}. \overline{z} + \overline{w}. \overline{x}. y. \overline{z} + \overline{w}. x. \overline{y}. \overline{z} + \overline{w}. x. y. \overline{z} + w. \overline{x}. \overline{y}. \overline{z} + w. \overline{x}. y. \overline{z} + w. x. \overline{y}. \overline{z}$$

Minimization using Kmap

$$f_2 = \sum (2, 3)$$

$$f = x.\bar{y} + x.y$$

$$f = x.(\bar{y} + y)$$

$$f = x$$

A Karnaugh map for a 2-variable function f2. The horizontal axis is labeled 'y' with values 0 and 1. The vertical axis is labeled 'x' with values 0 and 1. The map contains four cells: (0,0) with value 0, (0,1) with value 0, (1,0) with value 1, and (1,1) with value 1. A red oval encircles the two cells with value 1, and a red arrow points from the expression x.(y-bar + y) to this oval.

	y	0	1
x	0	0	0
1	1	1	1

Combine terms which differ in only one bit position. As a result, whatever is common remains.

		y	
		0	1
x	0	0	1
	1	0	1

$$f = \bar{x}.y + x.y$$

$$f = (\bar{x} + x).y$$

$$\Rightarrow f = y$$

		y	
		0	1
x	0	1	0
	1	1	0

$$\Rightarrow f = \bar{y}$$

		y	
		0	1
x	0	1	1
	1	0	0

$$\Rightarrow f = \bar{x}$$

$$F2 = \sum(1, 2, 3)$$

	y	0	1
x	0	0	1
	1	1	1

$$f = x.\bar{y} + x.y + \bar{x}.y$$

$$\begin{aligned} f &= x.(\bar{y} + y) + \bar{x}.y \\ &= x + \bar{x}.y \end{aligned}$$

$$\begin{aligned} f &= x + \bar{x}.y + x.y \\ &= x + (\bar{x} + x).y \\ &= x + y \end{aligned}$$

The idea is to cover all the 1's with as few and as simple terms as possible

3-variable minimization

x \ yz	00	01	11	10
0	1	0	1	0
1	0	1	1	0

$x.z$

$y.z$

$$f = \bar{x}.\bar{y}.\bar{z} + \bar{x}.y.z + x.y.z + x.\bar{y}.z$$

$$f = \bar{x}.\bar{y}.\bar{z} + y.z + x.z$$

3-variable minimization

x \ yz	00	01	11	10
0	1	0	0	1
1	0	1	1	0

$$f = \bar{x}.\bar{y}.\bar{z} + \bar{x}.y.\bar{z} + x.y.z + x.\bar{y}.z$$

$$\bar{x}.\bar{z}$$

$$x.z$$

$$f = \bar{x}.\bar{z} + x.z$$

3-variable minimization

x \ yz	00	01	11	10
0	0	0	0	0
1	1	1	1	1

$$f = x.\bar{y}.\bar{z} + x.\bar{y}.z + x.y.\bar{z} + x.y.z$$

$$x.\bar{y}$$





$$x.y$$

$$f = x.\bar{y} + x.y$$

x \ yz	00	01	11	10
0	0	0	0	0
1	1	1	1	1

$$f = x.(\bar{y} + y) = x$$

$$x$$

    

$$f = \bar{x} + \bar{z}$$

Can we do this ?

A Karnaugh map for a three-variable function f(x,y,z). The map is a 2x4 grid. The columns are labeled with yz values: 00, 01, 11, 10. The rows are labeled with x values: 0 and 1. The cells contain the following values: (0,00)=0, (0,01)=0, (0,11)=0, (0,10)=0; (1,00)=1, (1,01)=1, (1,11)=1, (1,10)=0. A red oval encircles the three 1s in the row where x=1, specifically the cells for yz=00, 01, and 11.

x \ yz	00	01	11	10
0	0	0	0	0
1	1	1	1	0

Note that each encirclement should represent a single product term. In this case it does not.

$$\begin{aligned} f &= \overline{x}.\overline{y}.\overline{z} + \overline{x}.\overline{y}.z + \overline{x}.y.\overline{z} \\ &= \overline{x}.y + \overline{x}.z \end{aligned}$$

We do not get a single product term.

In general we cannot make groups of 3 terms.

Can we use kmap with the following ordering of variables?

x \ yz	00	01	10	11
0	0	0	0	0
1	0	1	1	0

Can we combine these two terms into a single term ?

$$\begin{aligned}f &= \bar{x}.\bar{y}.z + x.y.\bar{z} \\ &= x.(\bar{y}.z + y.\bar{z})\end{aligned}$$

Note that no simplification is possible.
Kmap requires information to be represented


<div>yz x</div>		00	01	10	11
		0	1	0	1
0	0	1	0	1	
1	0	0	0	0	

These two terms can be combined into a single term but it is not easy to show that on the diagram.

$$\begin{aligned}
 f &= \bar{x}.\bar{y}.z + \bar{x}.y.z \\
 &= \bar{x}.(\bar{y} + y).z = \bar{x}.z
 \end{aligned}$$

Kmap requires information to be represented in such a way that it is easy to apply the principle $x + \bar{x} = 1$

4-variable minimization

 

$$f = \overline{w}.y.z + \overline{w}.x.z + w.\overline{y}.\overline{z} + \overline{w}.x.y.z + w.x.y.z$$

But is this the simplest expression ?


wx \ yz	00	01	11	10
00	1	0	1	0
01	0	1	1	0
11	1	0	0	1
10	1	0	0	0

wx \ yz	00	01	11	10
00	1	0	1	0
01	0	1	1	0
11	1	0	0	1
10	1	0	0	0

$$w \cdot x \cdot \bar{y} \cdot \bar{z} + w \cdot x \cdot y \cdot \bar{z} = w \cdot x \cdot \bar{z}$$

$$w \cdot \bar{x} \cdot \bar{y} \cdot \bar{z} + w \cdot x \cdot y \cdot \bar{z} = x \cdot y \cdot \bar{z}$$

4-variable minimization

 

$$f = \overline{w}. y. z + \overline{w}. x. z + w. \overline{y}. \overline{z} + w. x. \overline{z} + \overline{x}. \overline{y}. \overline{z}$$

Is this the best that we can do ?

Cover the 1's with minimum number of terms

wx \ yz	00	01	11	10
00	1	0	1	0
01	0	1	1	0
11	1	0	0	1
10	1	0	0	0

wx \ yz	00	01	11	10
00	1	0	1	0
01	0	1	1	0
11	1	0	0	1
10	1	0	0	0

$$f = \bar{w}.y.z + \bar{w}.x.z + w.\bar{y}.\bar{z} + w.x.\bar{z} + \bar{x}.\bar{y}.\bar{z}$$

$$f = \bar{w}.y.z + \bar{w}.x.z + w.x.\bar{z} + \bar{x}.\bar{y}.\bar{z}$$

4-variable minimization

wx \ yz	00	01	11	10
00	1	0	0	0
01	1	1	0	0
11	0	0	0	0
10	1	0	0	1

wx \ yz	00	01	11	10
00	1	0	0	0
01	1	1	0	0
11	0	0	0	0
10	1	0	0	1

$$f = \overline{w}.x.\overline{y} + w.\overline{x}.\overline{z} + \overline{w}.\overline{y}.\overline{z}$$

$$f = \overline{w}.x.\overline{y} + w.\overline{x}.\overline{z} + x.\overline{y}.\overline{z}$$

Groups of 4

$$\overline{y} \cdot z$$

wx \ yz	00	01	11	10
00	0	1	0	0
01	1	1	1	1
11	0	1	0	0
10	0	1	0	0

$$\overline{w} \cdot x$$

wx \ yz	00	01	11	10
00	0	0	0	0
01	0	1	1	0
11	0	1	1	0
10	0	1	1	0

$$x \cdot z$$

$$w \cdot z$$

wx \ yz	00	01	11	10
00	0	0	0	0
01	1	0	0	1
11	1	0	0	1
10	0	0	0	0

$\overline{x} \cdot z$

wx \ yz	00	01	11	10
00	0	1	1	0
01	0	0	0	0
11	0	0	0	0
10	0	1	1	0

$\overline{x} \cdot z$

wx \ yz	00	01	11	10
00	1	0	0	1
01	0	0	0	0
11	0	0	0	0
10	1	0	0	1

$\overline{\overline{x}} \cdot \overline{\overline{z}}$

wx \ yz	00	01	11	10
00	1	0	1	0
01	0	0	0	0
11	0	0	0	0
10	1	0	1	0

??

Groups of 8

wx \ yz	00	01	11	10
00	0	1	1	0
01	0	1	1	0
11	0	1	1	0
10	0	1	1	0

z

wx \ yz	00	01	11	10
00	0	0	0	0
01	1	1	1	1
11	1	1	1	1
10	0	0	0	0

x

wx \ yz	00	01	11	10
00	1	0	0	1
01	1	0	0	1
11	1	0	0	1
10	1	0	0	1

\bar{z}

wx \ yz	00	01	11	10
00	1	1	1	1
01	0	0	0	0
11	0	0	0	0
10	1	1	1	1


\bar{x}

Examples

wx \ yz	00	01	11	10
00	0	1	0	1
01	1	1	1	1
11	1	1	1	1
10	0	0	0	1

wx \ yz	00	01	11	10
00	0	1	0	1
01	1	1	0	1
11	1	1	1	1
10	0	0	0	1

Don't care terms

 

Y_3

	cd	00	01	11	10
ab					
00		0	0	1	0
01		0	0	0	0
11		x	x	x	x
10		0	0	x	x

$$y_3 = \bar{a}.\bar{b}.c.d$$

a	b	c	d	y_0	y_1	y_2	y_3	y_4	y_5	y_6	y_7	y_8	y_9
0	0	0	0	1	0	0	0	0	0	0	0	0	0
0	0	0	1	0	1	0	0	0	0	0	0	0	0
0	0	1	0	0	0	1	0	0	0	0	0	0	0
0	0	1	1	0	0	0	1	0	0	0	0	0	0
0	1	0	0	0	0	0	0	1	0	0	0	0	0
0	1	0	1	0	0	0	0	0	1	0	0	0	0
0	1	1	0	0	0	0	0	0	0	1	0	0	0
0	1	1	1	0	0	0	0	0	0	0	1	0	0
1	0	0	0	0	0	0	0	0	0	0	0	1	0
1	0	0	1	0	0	0	0	0	0	0	0	0	1
1	0	1	0	x	x	x	x	x	x	x	x	x	x
1	0	1	1	x	x	x	x	x	x	x	x	x	x
1	1	0	0	x	x	x	x	x	x	x	x	x	x
1	1	0	1	x	x	x	x	x	x	x	x	x	x
1	1	1	0	x	x	x	x	x	x	x	x	x	x
1	1	1	1	x	x	x	x	x	x	x	x	x	x

Don't care terms can be chosen as 0 or 1.
Depending on the problem, we can choose the don't care term as 1 and use it to obtain a simpler Boolean expression

Y_3

cd \ ab	00	01	11	10
00	0	0	1	0
01	0	0	0	0
11	x	x	x	x
10	0	0	x	x

$$y_3 = \bar{b}.c.d$$

Don't care terms should only be included in encirclements if it helps in obtaining a larger grouping or smaller number of groups.

Minimization of Product of Sum Terms using Kmap

x \ y	0	1
0	0	1
1	1	1

$$\begin{aligned}f &= x + \bar{x}.y + x.y \\&= x + (\bar{x} + x).y \\&= x + y\end{aligned}$$

x \ y	0	1
0	0	1
1	1	1

$$f = x + y$$

x \ y	0	1
0	0	1
1	0	1

$$f = y$$

		y	
		0	1
x	0	1	0
	1	1	0

$$\Rightarrow f = \bar{y}$$

		y	
		0	1
x	0	1	1
	1	0	0

$$\Rightarrow f = \bar{x}$$

$$\bar{x} + z$$

		yz			
		00	01	11	10
x	0	1	0	0	1
	1	0	1	1	0

$$x + \bar{z}$$

$$f = (\bar{x} + z) \cdot (x + \bar{z})$$

$$\Rightarrow f = \bar{x} \cdot \bar{z} + x \cdot z$$

$$x + y + z$$

wx \ yz	00	01	11	10
00	0	1	0	1
01	1	1	1	1
11	1	0	1	1
10	0	0	0	0

$$x + \bar{y} + \bar{z}$$

$$\bar{w} + y + \bar{z}$$

$$\bar{w} + x$$

$$f = (x + y + z) \cdot (x + \bar{y} + \bar{z}) \cdot (\bar{w} + y + \bar{z}) \cdot (\bar{w} + x)$$

Example


Obtain the minimized PoS by suitably using don't care terms

yz \ wx	00	01	11	10
00	1	x	0	1
01	1	0	1	1
11	0	x	1	1
10	1	x	1	x

$$f = (x + w + \bar{z}).(\bar{x} + \bar{w} + y).(y + \bar{z})$$

Design Flow

System Description

 

Truth Table

x	y	z	f
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1


Boolean Expression

$$f = \bar{x}.\bar{y}.z + \bar{x}.y.z + x.\bar{y}.z + x.y.z$$

**Minimized
Boolean Expression**


$$\Rightarrow f = \bar{x}.\bar{z} + x.z$$

Gate Netlist

 

Mapping of Boolean expression to a Network of gates available in the library
 
$$y = \overline{x_1} \cdot \overline{x_2} \cdot x_3 + \overline{x_1} \cdot x_2 \cdot x_3 + x_1 \cdot \overline{x_2} \cdot x_3 + x_1 \cdot x_2 \cdot x_3$$



Library of available Gates		Cost
Inverter		1
Two input NAND		2
Three input NAND		3
AND-OR-Invert	$Y = \overline{AB + C}$	3

IMPLEMENTATION USING SPECIFIC GATES



Implementation using only NAND gates




$$\overline{x \cdot x} = \overline{x}$$

$$\overline{x \cdot y} = \overline{x} \cdot \overline{y}$$

$$\overline{\overline{x \cdot y}} = x + y$$

  A SoP expression is easily implemented with NAND gates. $f = a.b + c.d + g.h$





   


There is a one-to-one mapping between AND-OR network and NAND network

Often there is lot of further optimization that can be done

  Consider implementation of XOR gate $f = \bar{A}.B + A.\bar{B}$


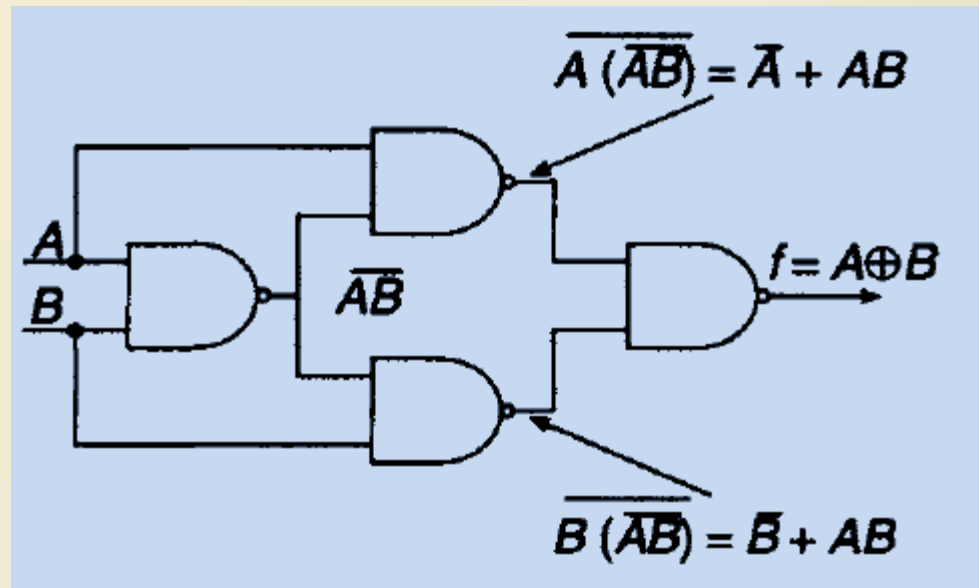
$$\begin{aligned} f &= \bar{A}.B + B.\bar{B} + A.\bar{B} + A.\bar{A} \\ &= B(\bar{A} + \bar{B}) + A(\bar{A} + \bar{B}) \end{aligned}$$



Implementation using only NOR gates

$$\overline{x + x} = \overline{x}$$

$$\overline{x + y}$$

$$x + y$$

$$\overline{x}$$




$$\overline{y}$$

$$f = \overline{\overline{x + \overline{y}}} = x.y$$

To implement using NOR gates, it is easiest to start with minimized Boolean expression in POS form

$$f = (a + b).(c + d).(g + h)$$

$$f = (a + b).(c + d).(g + h)$$

   

There is a one-to-one mapping between OR-AND network and NOR network



To implement SoP expression using NOR gates, determine first the corresponding PoS expression and then follow the procedure outlined earlier

Implement $f(x,y,z) = \bar{x} \cdot \bar{z} + x \cdot z$ using NOR gates

↓

$x \backslash yz$	00	01	11	10
0	1	0	0	1
1	0	1	1	0

  
$$\Rightarrow f = (\bar{x} + z) \cdot (x + \bar{z})$$




Similarly PoS expression can be implemented as NAND network by first converting it to SoP expression and then following the procedure outlined earlier

COMBINATIONAL CIRCUIT DESIGN

Digital Circuits

 


Combinational Circuits

 


Output is determined by current values of inputs only.

Sequential Circuits

 


Output is determined in general by current values of inputs and past values of inputs/outputs as well.

Design of Complex Combinational circuits

 


$A_7A_6...A_0$	$B_7B_6...B_0$	$S_7S_6...S_0$	C
00...0	00...0	00...0	0
00...1	00...0	00...1	0
00...0	00...1	00...1	0
⋮	⋮	⋮	⋮

Truth table has 2^{16} entries

 


This design approach becomes difficult to use

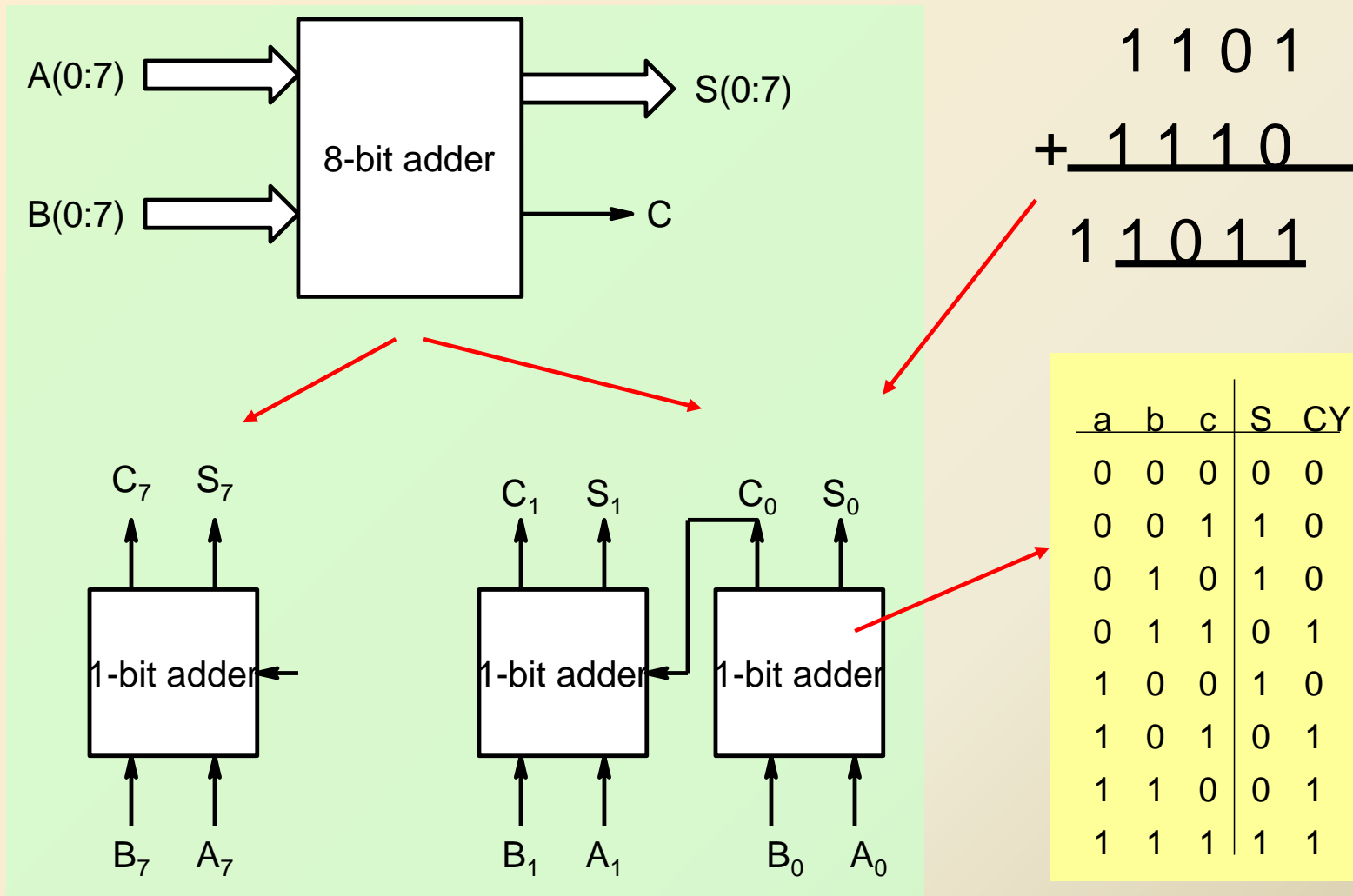Design system as a network of sub-systems that are of manageable size and can be implemented using the earlier approach of truth table, minimization etc.



General Approach

 


There are certain sub-systems or blocks that are used quite often such as :

 
1. **decoders, encoders**
2. **Multiplexers**
3. **Adder/Subtractors, Multipliers**
4. **Comparators**
5. **Parity Generators**
6.

Decoders

Maps a smaller number of inputs to a larger set of outputs in general





B	A	Y_0	Y_1	Y_2	Y_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

 


b	a	Y_0	Y_1	Y_2	Y_3
0	0	0	1	1	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	1	1	1	0

Active Low


Example

  

Decoder with Enable Input

 


E	B	A	Y ₀	Y ₁	Y ₂	Y ₃
0	x	x	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

 


E	B	A	Y ₀	Y ₁	Y ₂	Y ₃
1	x	x	0	0	0	0
0	0	0	1	0	0	0
0	0	1	0	1	0	0
0	1	0	0	0	1	0
0	1	1	0	0	0	1

Decoder: gate Implementation

 


E	B	A	Y ₀	Y ₁	Y ₂	Y ₃
0	x	x	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
 
$$Y_0 = E \cdot \overline{B} \cdot \overline{A} ; Y_1 = E \cdot \overline{B} \cdot A ; Y_2 = E \cdot B \cdot \overline{A} ; Y_3 = E \cdot B \cdot A$$




A n to 2^n decoder is a minterm generator

x	y	min term
0	0	$\bar{x} \cdot \bar{y}$ m0
0	1	$\bar{x} \cdot y$ m1
1	0	$x \cdot \bar{y}$ m2
1	1	$x \cdot y$ m3

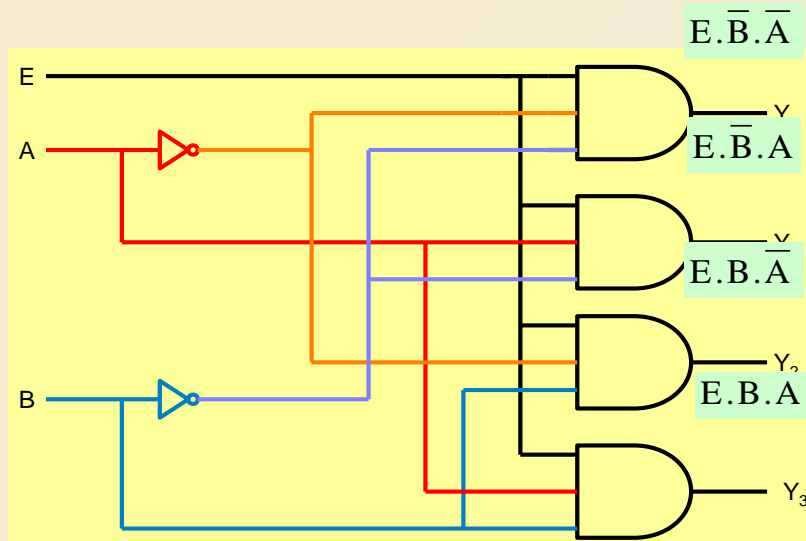


It can be used to implement any combinational circuit

B	A	f_1
0	0	0
0	1	1
1	0	1
1	1	0

 

Implementation of a 3-variable function with a 3-to-8 decoder



C	B	A	f
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

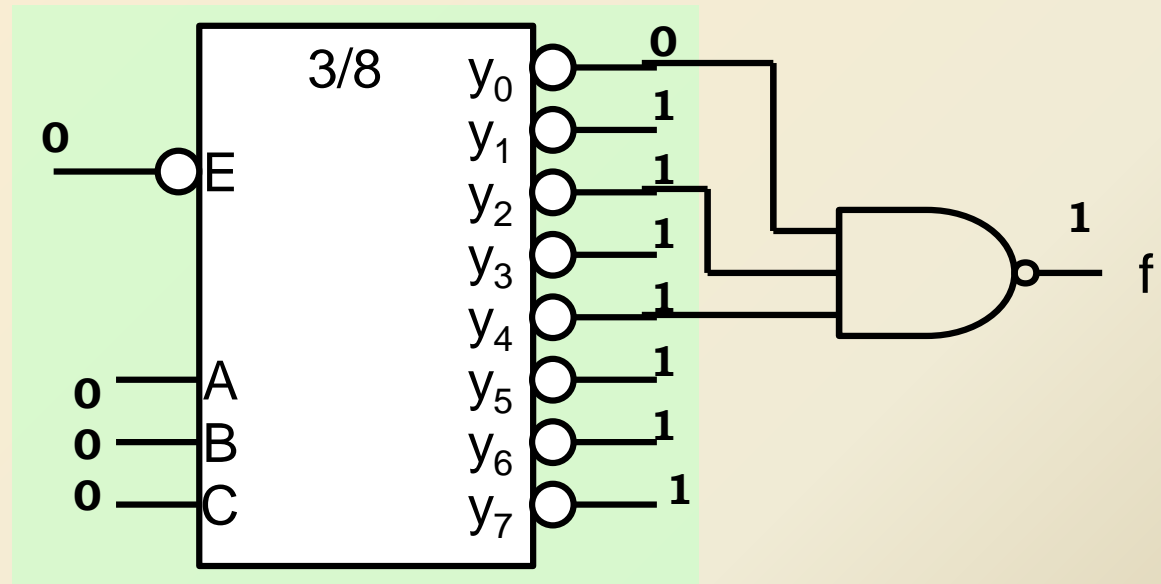

Although it is easy to implement any combinational circuit with this method , it is often very inefficient in terms of gate utilization. Note that this method does not require any minimization.


Implementing larger decoders using simpler ones.

3/8 decoder using 2/4 decoders

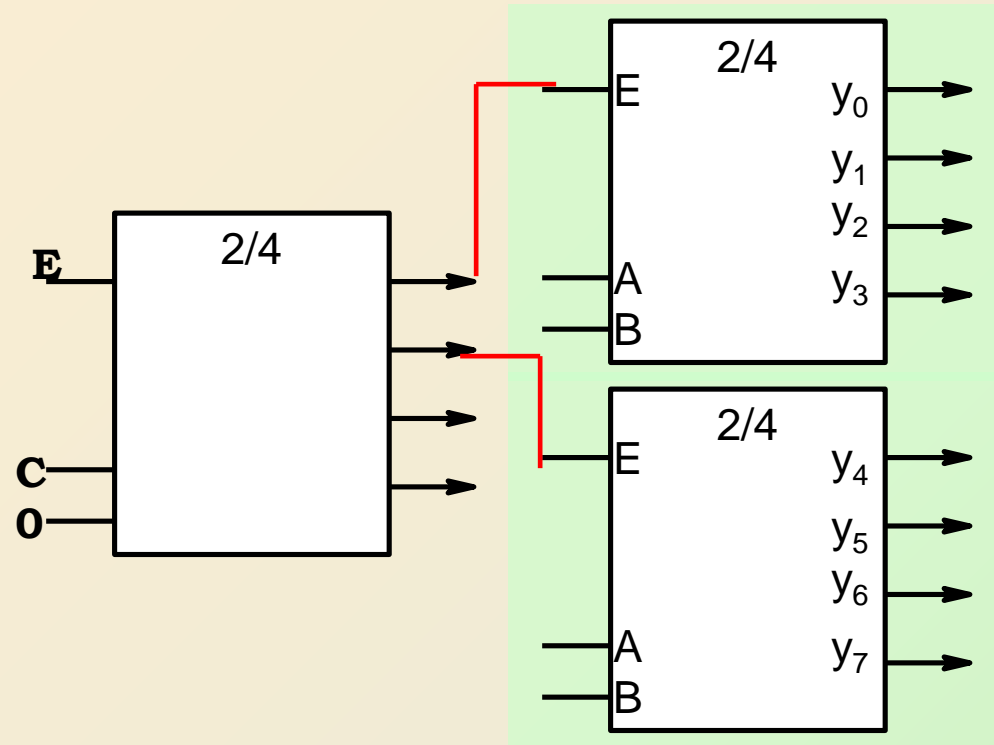 







How many 2/4 decoders are required to implement a 4/16 decoder ?

E	C	B	A	y_0	y_1	y_2	y_3	y_4	y_5	y_6	y_7
0	x	x	x	0	0	0	0	0	0	0	0
1	0	0	0	1	0	0	0	0	0	0	0
1	0	0	1	0	1	0	0	0	0	0	0
1	0	1	0	0	0	1	0	0	0	0	0
1	0	1	1	0	0	0	1	0	0	0	0
1	1	0	0	0	0	0	0	1	0	0	0
1	1	0	1	0	0	0	0	0	1	0	0
1	1	1	0	0	0	0	0	0	0	1	0
1	1	1	1	0	0	0	0	0	0	0	1


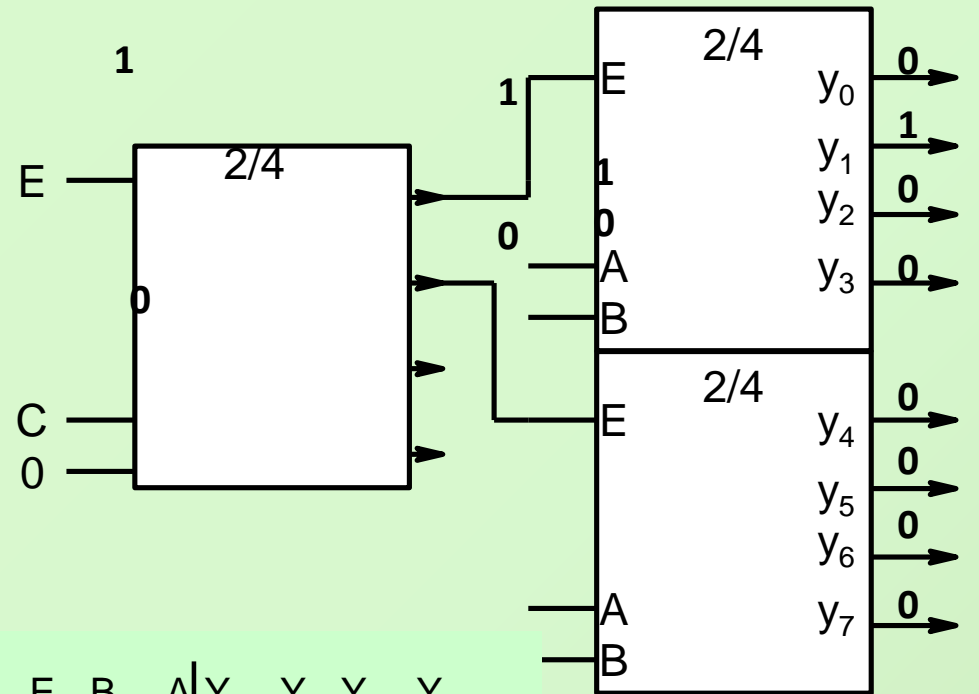


E	B	A	Y_0	Y_1	Y_2	Y_3
0	x	x	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

Seven segment decoder

      


Seven segment decoder

  


Dec or Function	Input					Output						
	D	C	B	A	BI	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	1	0
1	0	0	0	1	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	1	0	0	1
4	0	1	0	0	1	0	1	1	0	0	1	1
5	0	1	0	1	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	0	1	1	1	1	1
7	0	1	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	1	0	0	1	1
10	1	0	1	0	1	0	0	0	1	1	0	1
11	1	0	1	1	1	0	0	1	1	0	0	1
12	1	1	0	0	1	0	1	0	0	0	1	1
13	1	1	0	1	1	1	0	0	1	0	1	1
14	1	1	1	0	1	0	0	0	1	1	1	1
15	1	1	1	1	1	0	0	0	0	0	0	0
BI	x	x	x	x	0	0	0	0	0	0	0	0

DC \ BA					
		00	01	11	10
DC	00	1	0	1	1
	01	0	1	1	0
	11	0	1	0	0
	10	1	1	0	0
	10	1	1	0	0

 


7449 BCD to seven segment decoder

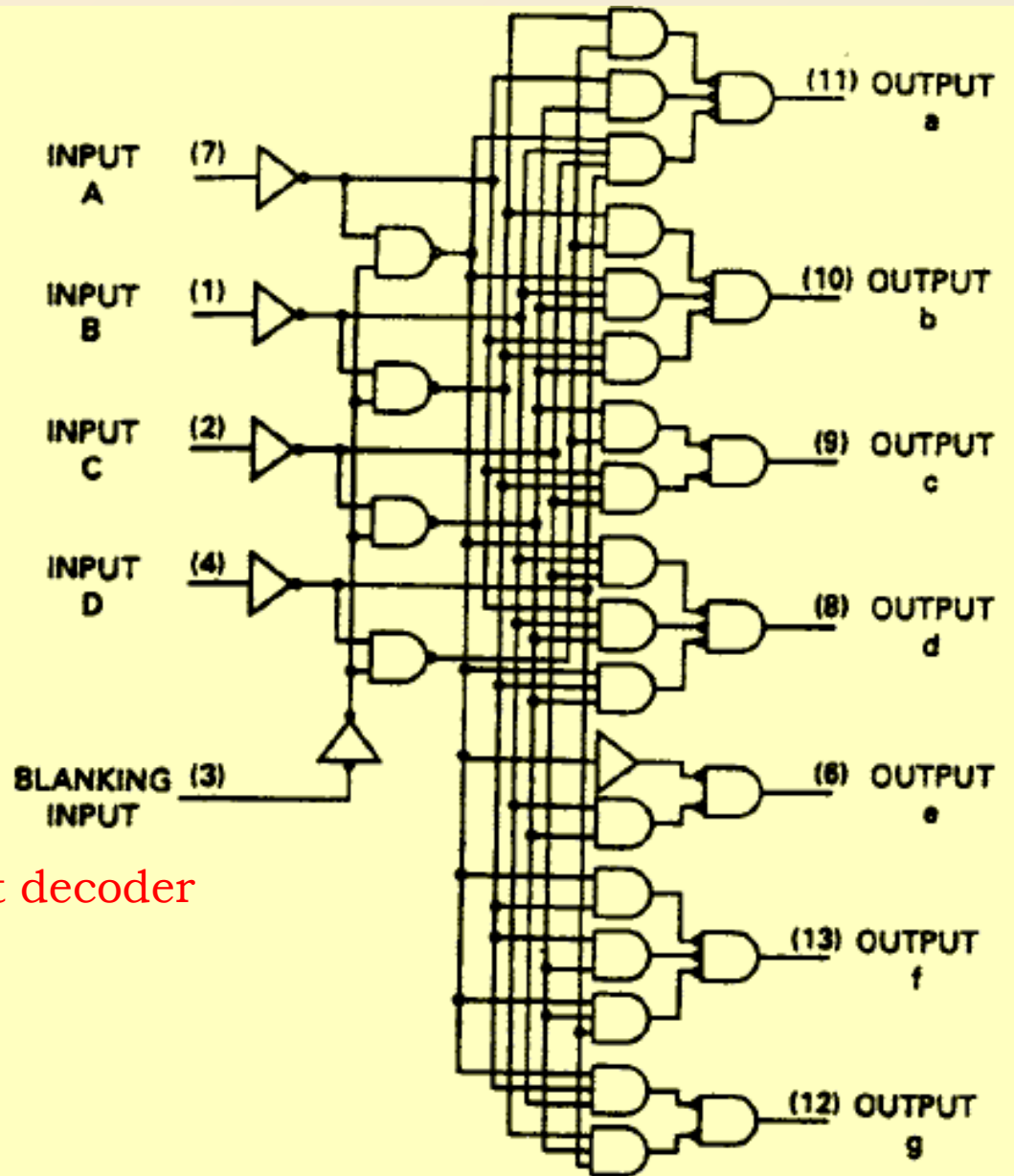

Encoders

 An encoder performs the inverse operation of a decoder.




d_3	d_2	d_1	d_0	B	A
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

$d_1 d_0$	00	01	11	10
$d_3 d_2$	00	0		1
01	0			
11				
10	1			


$$A = \overline{d_2} \ \overline{d_0}$$

$d_1 d_0$	00	01	11	10
$d_3 d_2$	00	0		0
01	1			
11				
10	1			

$$B = \overline{d_1} \ \overline{d_0}$$

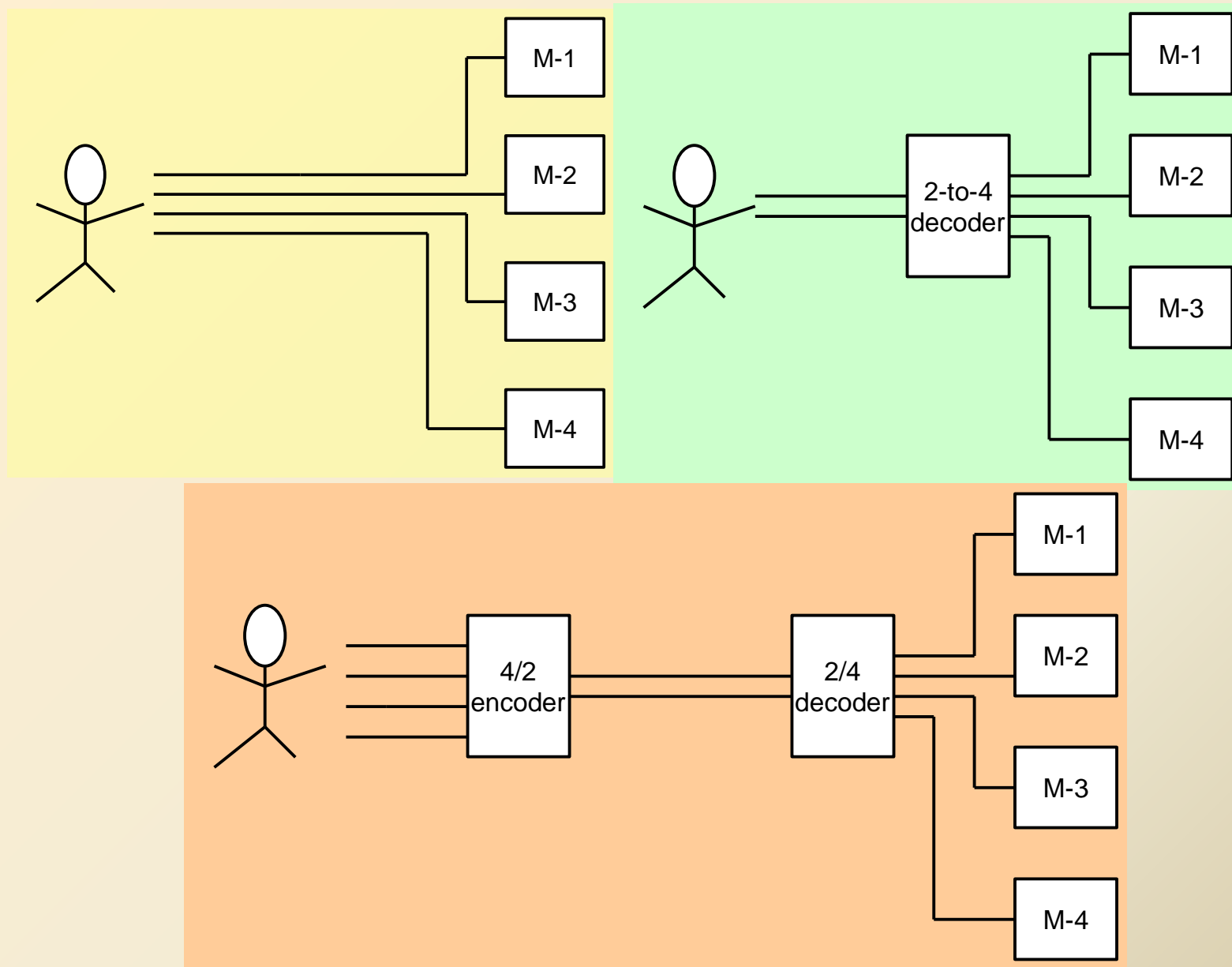

Priority Encoders

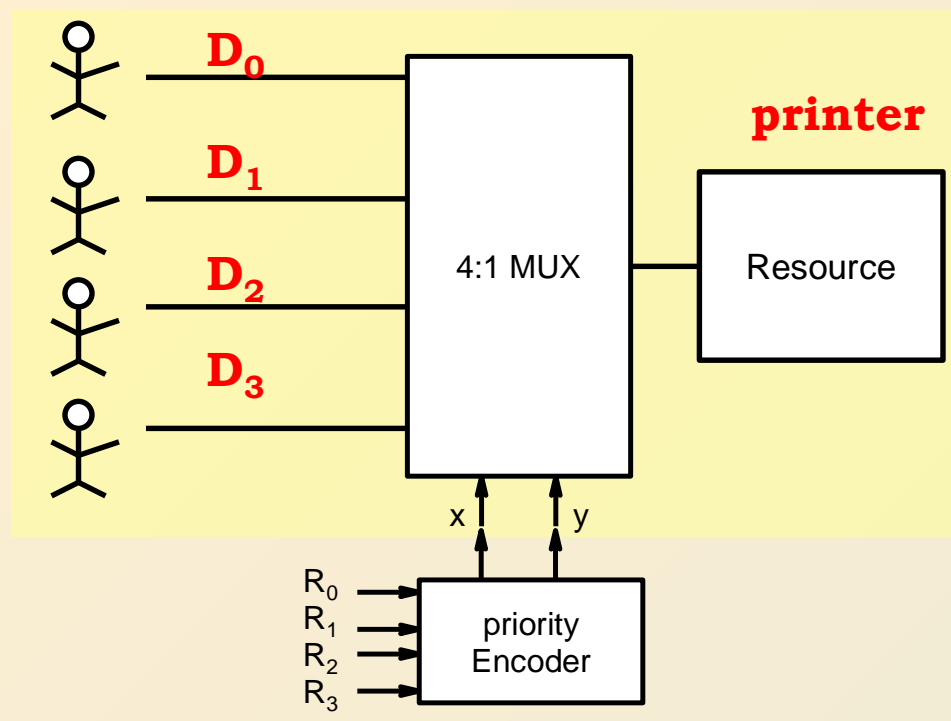

Priority is 3,2,1,0 with user 3 having the highest priority

X, Y have to be determined based on this priority order and the requests to use the resource.

R_0	R_1	R_2	R_3	x	y
0	0	0	0	x	x
1	0	0	0	0	0
x	1	0	0	0	1
x	x	1	0	1	0
x	x	x	1	1	1

		X			
R_1R_0	R_3R_2	00	01	11	10
00	00	0		0	0
01	00	1	1	1	1
11	00	1	1	1	1
10	00	1	1	1	1

$$x = R_2 + R_3$$

		Y			
R_1R_0	R_3R_2	00	01	11	10
00	00		0	1	1
01	00	0	0	0	0
11	00	1	1	1	1
10	00	1	1	1	1

$$y = R_1 \overline{R_2} + R_3$$

Gray Codes

decimal	Natural Binary	Gray
0	0000	0000
1	0001	0001
2	0010	0011
3	0011	0010
4	0100	0110
5	0101	0111
6	0110	0101
7	0111	0100
8	1000	1100
9	1001	1101
10	1010	1111
11	1011	1110
12	1100	1010
13	1101	1011
14	1110	1001
15	1111	1000

In the case of natural binary code:

0111-1111-1000 0111-0000-1000

In the case of Gray code, no such problem occurs.

1-bit change as one goes from one code word to the next.

ASCII: American Standard Code for information interchange

Hex	ASCII	Hex	ASCII	Hex	ASCII	Hex	ASCII	Hex	ASCII	Hex	ASCII	Hex	ASCII	Hex	ASCII
00	NUL	10	DLE	20	SP	30	0	40	Ⓐ	50	P	60	`	70	p
01	SOH	11	DC ₁	21	!	31	1	41	A	51	Q	61	a	71	q
02	STX	12	DC ₂	22	"	32	2	42	B	52	R	62	b	72	r
03	ETX	13	DC ₃	23	£(#)	33	3	43	C	53	S	63	c	73	s
04	EOT	14	DC ₄	24	\$	34	4	44	D	54	T	64	d	74	t
05	ENQ	15	NAK	25	%	35	5	45	E	55	U	65	e	75	u
06	ACK	16	SYN	26	&	36	6	46	F	56	V	66	f	76	v
07	BEL	17	ETB	27	'	37	7	47	G	57	W	67	g	77	w
08	BS	18	CAN	28	(38	8	48	H	58	X	68	h	78	x
09	HT	19	EM	29)	39	9	49	I	59	Y	69	i	79	y
0A	LF	1A	SUB	2A	*	3A	:	4A	J	5A	Z	6A	j	7A	z
0B	VT	1B	ESC	2B	+	3B	;	4B	K	5B	[6B	k	7B	{
0C	FF	1C	FS	2C	,	3C	<	4C	L	5C	\	6C	l	7C	
0D	CR	1D	GS	2D	-	3D	=	4D	M	5D]	6D	m	7D	}
0E	SO	1E	RS	2E	.	3E	>	4E	N	5E	^	6E	n	7E	~
0F	SI	1F	US	2F	/	3F	?	4F	O	5F	_	6F	o	7F	DEL


Parity

Extra bits are added to aid in error detection and correction


Decimal	Binary	Even parity	Odd parity
0	000	0000	0001
1	001	0011	0010
2	010	0101	0100
3	011	0110	0111
4	100	1001	1000
5	101	1010	1011
6	110	1100	1101
7	111	1111	1110


A 1-bit error changes the parity and thus can be detected

Multiplexers

 


S	y
0	I_0
1	I_1

 


 

S_1	S_0	y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

 

 
Mux is often used when resources have to be shared



S_1	S_0	$y =$
0	0	$a+c$
0	1	$a+d$
1	0	$b+c$
1	1	$b+d$

Implementing Boolean expressions using Multiplexers
 
$$y = x_1 \overline{x_2} + \overline{x_1} x_2$$




x_1	x_2	y
0	0	0
0	1	1
1	0	1
1	1	0

$y = x_2$ when $x_1 = 0$

$y = \overline{x_2}$ when $x_1 = 1$

$$F(x, y, z) = \sum (1, 2, 6, 7)$$

 A 3 variable function can be implemented with a 4:1 mux with 2 select lines



x	y	z	F
0	0	0	0
1	0	0	0
0	0	1	1
1	0	1	0
0	1	0	1
1	1	0	1
0	1	1	0
1	1	1	1

$F = 0$ when $yz = 00$


$F = \overline{x}$ when $yz = 01$

$F = 1$ when $yz = 10$

$F = x$ when $yz = 11$

Mux is more efficient way of implementing combinational circuits as compared to decoders.


Mux. expansion

 


E	S	y
0	x	0
1	0	I_0
1	1	I_1

S_1	S_0	y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

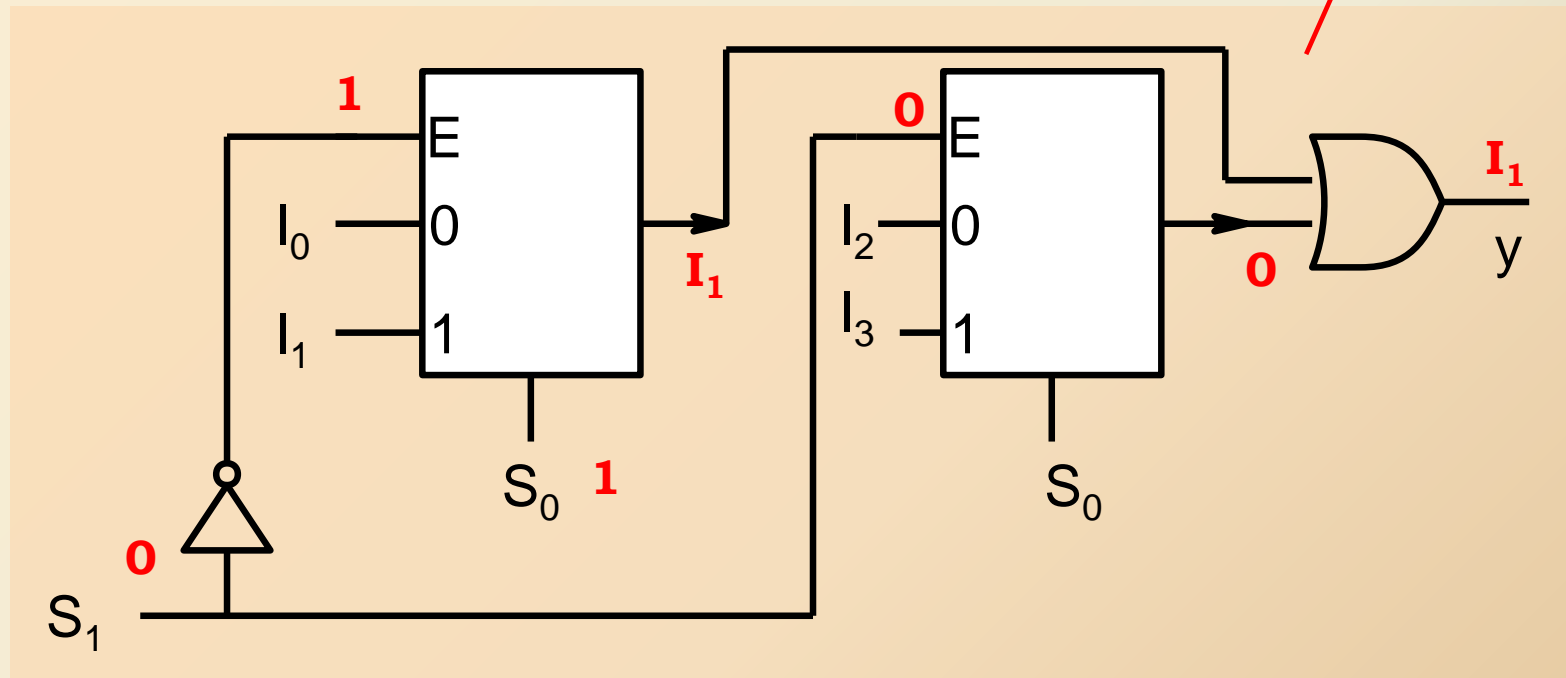A red arrow points from the $(S_1, S_0) = (1, 1)$ row to the output I_3 in the diagram below.




Mux. expansion



 


E	S	y
0	x	0
1	0	I_0
1	1	I_1

S_1	S_0	y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

 


DeMultiplexer

 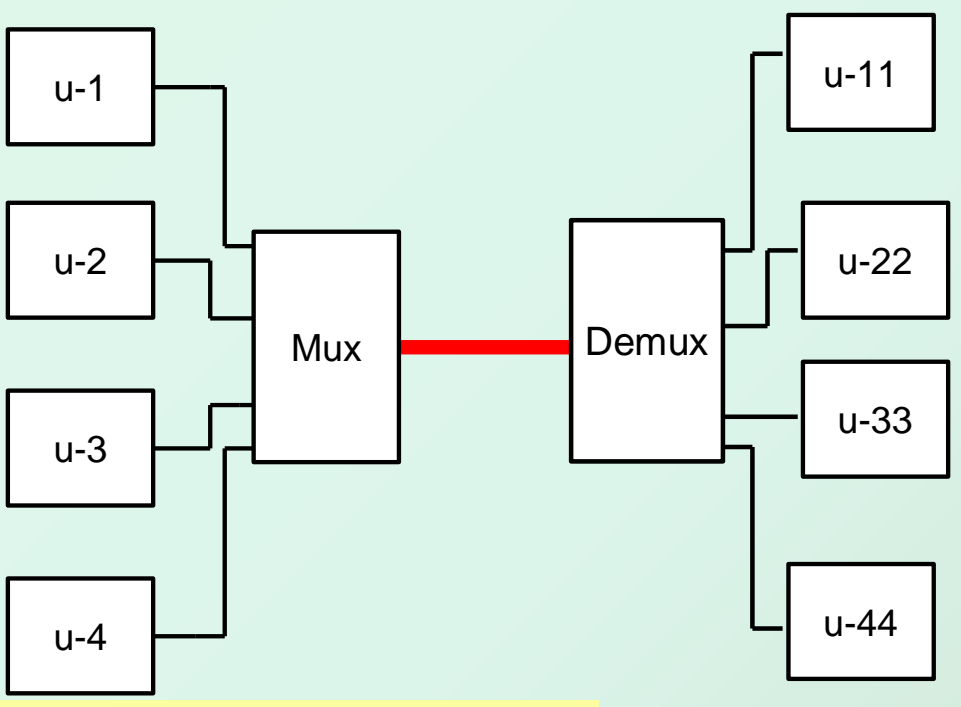 


S_1	S_0	y_0	y_1	y_2	y_3
0	0	x	0	0	0
0	1	0	x	0	0
1	0	0	0	x	0
1	1	0	0	0	x


 
Demultiplexer is very much like a decoder




S ₁	S ₀	y ₀	y ₁	y ₂	y ₃
0	0	x	0	0	0
0	1	0	x	0	0
1	0	0	0	x	0
1	1	0	0	0	x

 





E	B	A	Y ₀	Y ₁	Y ₂	Y ₃
0	x	x	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

  


Comparator

 


$A_3A_2A_1A_0$	$B_3B_2B_1B_0$	A<B	A>B	A=B
0000	0000	0	0	1
0000	0001	1	0	0
0001	0000	0	1	0
⋮	⋮	⋮	⋮	⋮

    


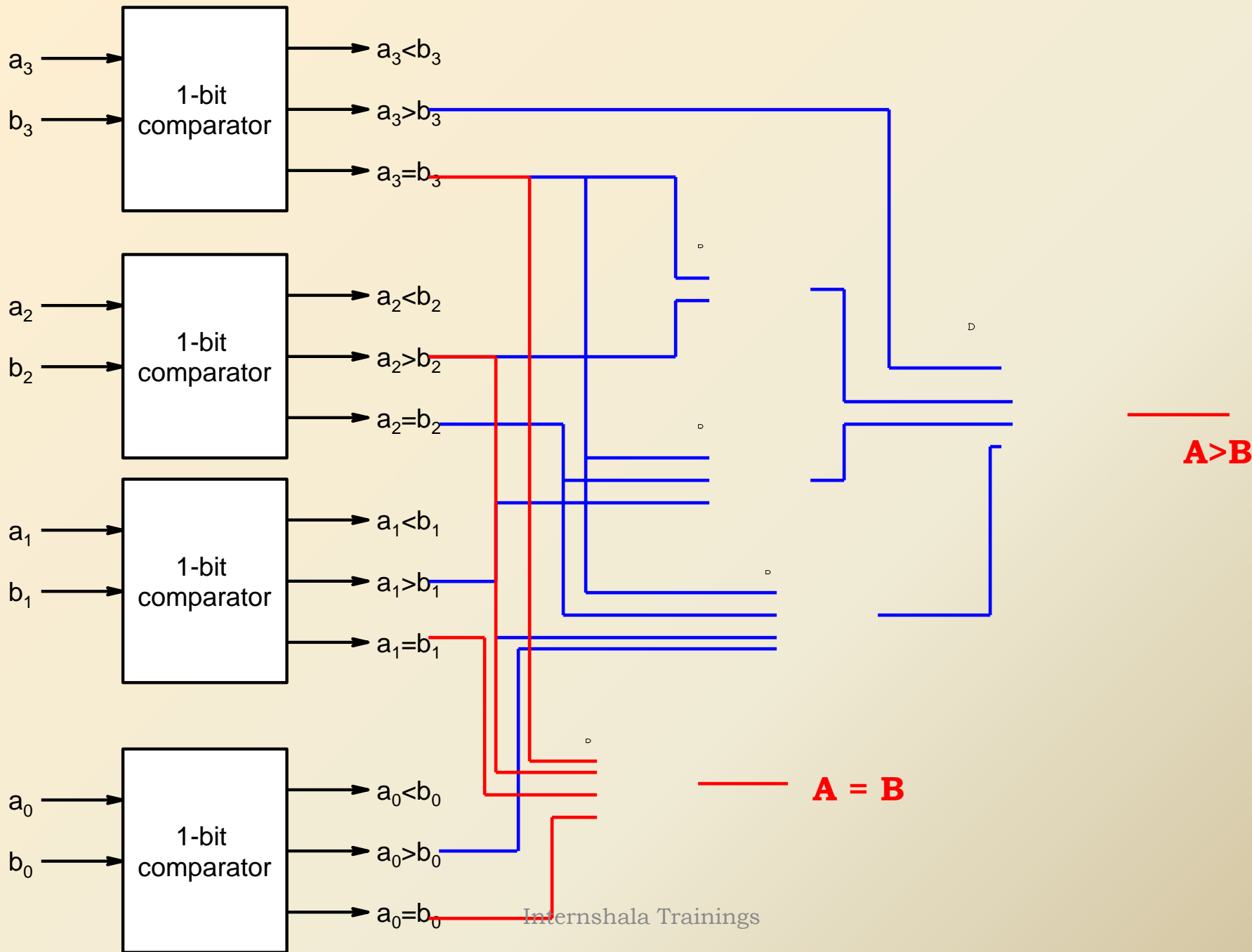




Adder/Subtractor

 

a	b	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 

$$S = \bar{a}.b + a.\bar{b}; C = a.b$$

   

a	b	C_{in}	S	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


$$S = \bar{\bar{a}}.\bar{b}.c_{in} + \bar{a}.b.\bar{c}_{in} + a.\bar{b}.\bar{c}_{in} + a.b.c_{in}; C_{out} = a.b + a.c_{in} + b.c_{in}$$

$$S = \bar{a}.\bar{b}.c_{in} + \bar{a}.b.\bar{c}_{in} + a.\bar{b}.\bar{c}_{in} + a.b.c_{in}$$


$$S = C_{in} \oplus (a \oplus b)$$

$$C_{out} = a.b + a.C_{in} + b.C_{in}$$
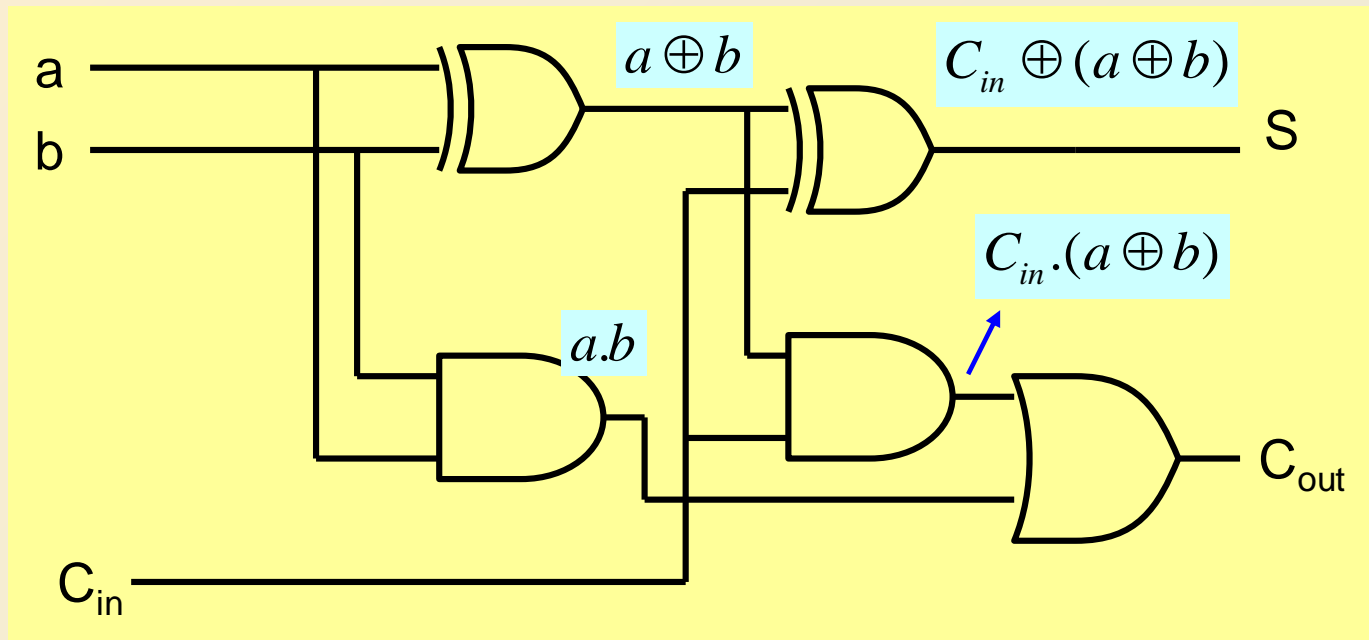
$$C_{out} = C_{in} (a.\bar{b} + \bar{a}.b) + a.b = C_{in} . (a \oplus b) + a.b$$




4-bit Adder

 

A ₃ A ₂ A ₁ A ₀	B ₃ B ₂ B ₁ B ₀	S ₃ S ₂ S ₁ S ₀	C _{out}
0000	0000	0000	1
0000	0001	0001	0
0001	0000	0001	0
⋮	⋮	⋮	⋮
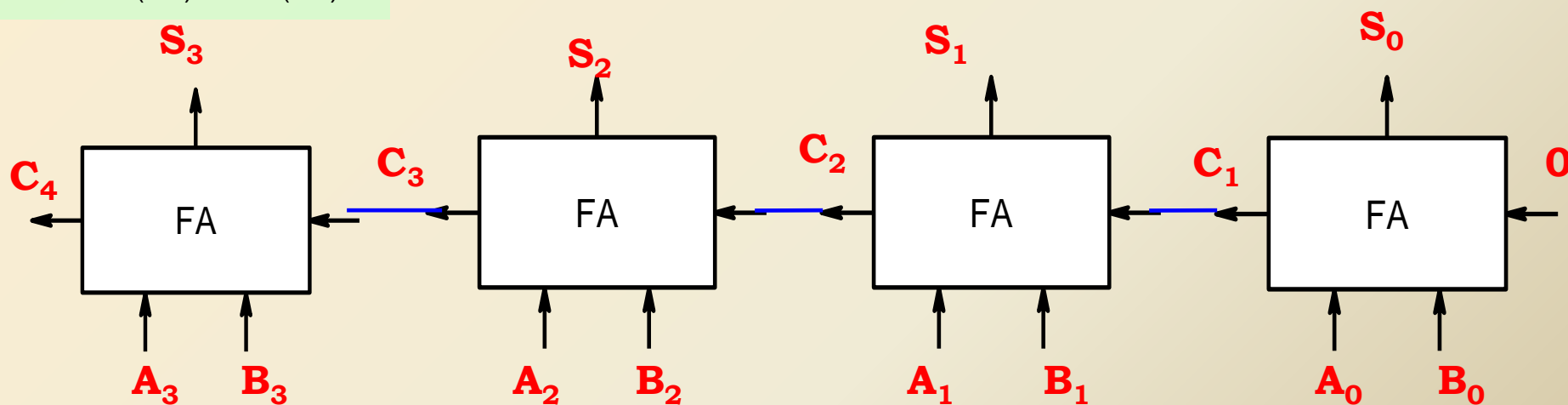
$$\begin{array}{r} C_3 C_2 C_1 \\ A_3 A_2 A_1 A_0 \\ B_3 B_2 B_1 B_0 \\ \hline C_4 S_3 S_2 S_1 S_0 \end{array}$$




Ripple Carry Adder (20 gate circuit)

Subtraction

$A - B = A + 2\text{'s complement of } B$


$A - B = A + 1\text{'s complement of } B + 1$

$$A - B = A + \overline{B} + 1$$


 


One needs add a circuit for predicting errors resulting from overflow

Adder/Subtractor

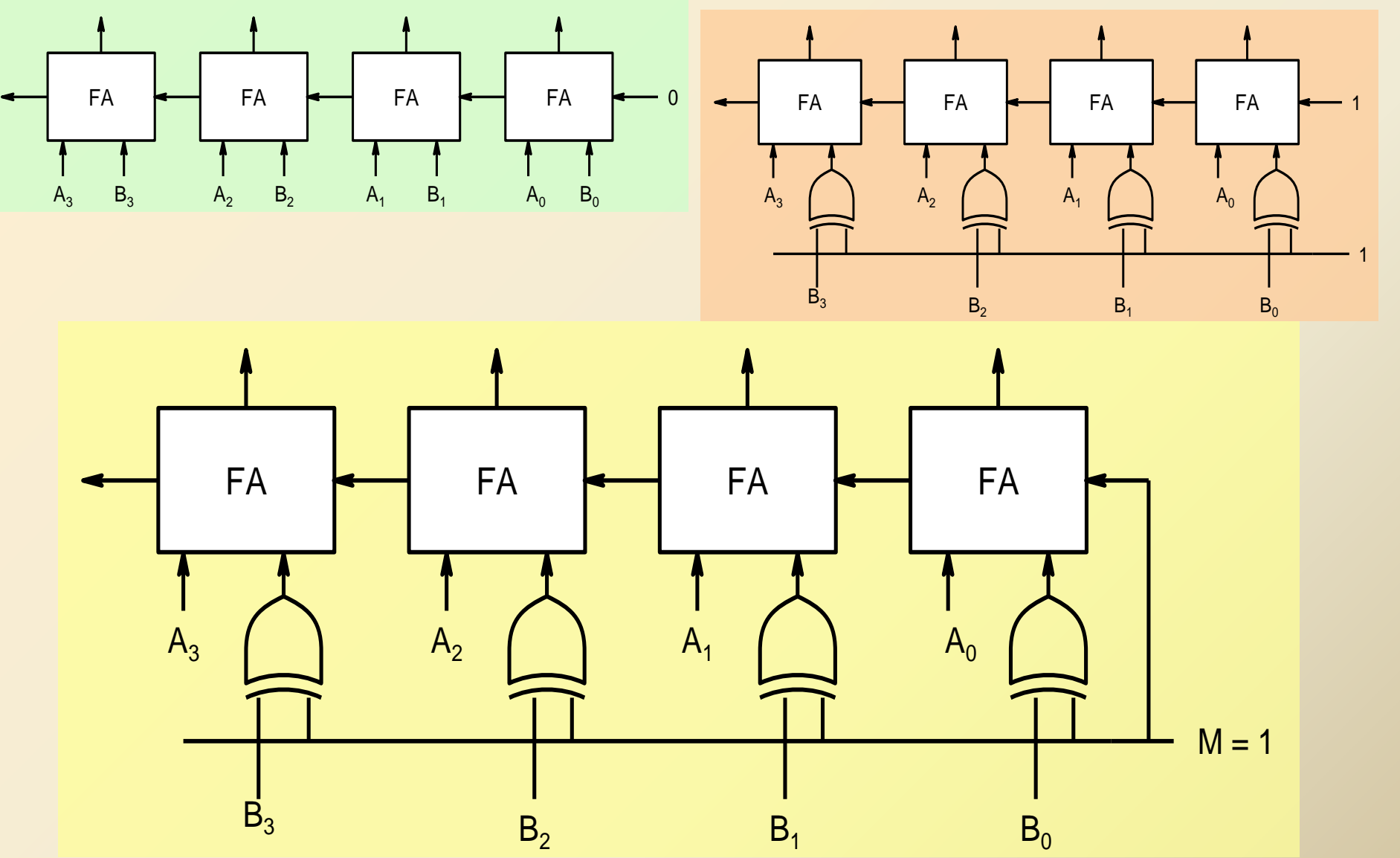


Multiplier

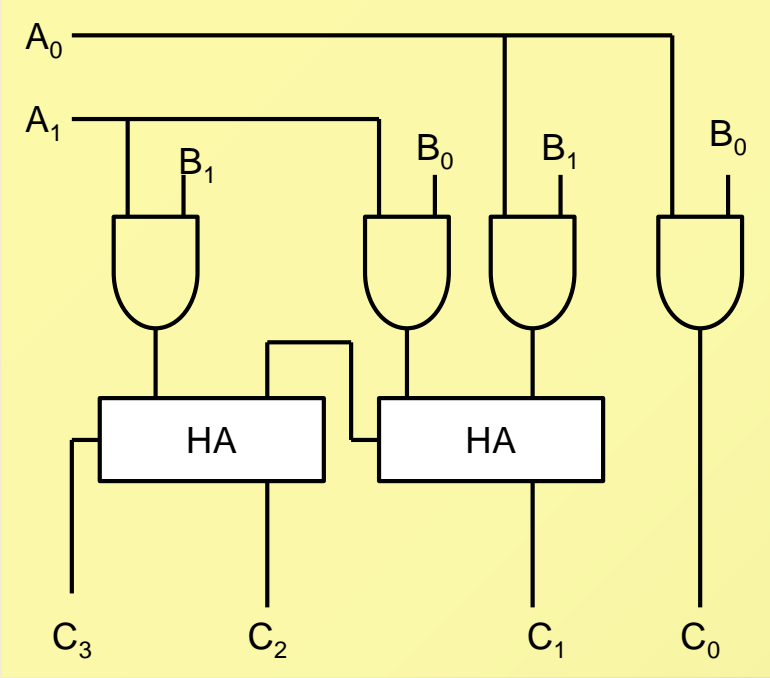 


SEQUENTIAL CIRCUITS

Digital Circuits

 


Combinational Circuits

 


Output is determined by current values of inputs only.

Sequential Circuits

 

Output is determined in general by current values of inputs and past values of inputs/outputs as well.

NOR SR Latch

 


$Q = 1; \bar{Q} = 0$ Set State

$Q = 0; \bar{Q} = 1$ Reset State

S	R	Q	\bar{Q}	State
1	0	1	0	SET

NOR SR Latch

 


$Q = 1; \bar{Q} = 0$ Set State


$Q = 0; \bar{Q} = 1$ Reset State

S	R	Q	\bar{Q}	State
1	0	1	0	SET
0	1	0	1	RESET

HOLD State



 





S	R	Q	\overline{Q}	State
1	0	1	0	SET
0	1	0	1	RESET
0	0	Q	\overline{Q}	HOLD
1	1	0	0	INVALID

 

Both the outputs are well defined and 0. the first problem is that we do not get complementary output.

 
 
 
A more serious problem occurs when we switch the latch to the hold state by changing RS from $11 \rightarrow 00$. Suppose the inputs do not change simultaneously and we get the situation $11 \rightarrow 01^* \rightarrow 00$



   

$Q = 1$

 
 
 
Suppose the inputs change as $RS = 11 \rightarrow 10^* \rightarrow 00$



$Q = 0$

So although output is well defined when we apply $RS = 11$, it becomes unpredictable once we switch the latch to hold state by applying $RS = 00$. That is why $RS = 11$ is not used as an input combination.

 
 
 
The error can occur also due to unequal gate delays.



Q = 1


Suppose gate-1 is faster

   On the other hand suppose that gate-2 is faster.




Again the output is unpredictable in general Q = 0

NAND Latch

 


S	R	Q	\overline{Q}	State
0	1	1	0	SET
1	0	0	1	RESET
1	1	Q	\overline{Q}	HOLD
0	0	1	1	INVALID

RS NAND Latch with Enable

 


Hold State

 


Enable	S	R	Q	\overline{Q}	State
0	x	x	Q	\overline{Q}	Hold
1	1	0	1	0	Set
1	0	1	0	1	Reset
1	0	0	Q	\overline{Q}	Hold
1	1	1	0	0	Invalid

D latch


 


Enable	S	R	Q	\bar{Q}	State
0	x	x	Q	\bar{Q}	Hold
1	1	0	1	0	Set
1	0	1	0	1	Reset
1	0	0	Q	\bar{Q}	Hold
1	1	1	0	0	Invalid

 

If $EN = 1$ then $Q = D$ otherwise the latch is in Hold state



Synchronous Sequential Circuits

  



Data is stable when clock is high

$X(n)$


Example

 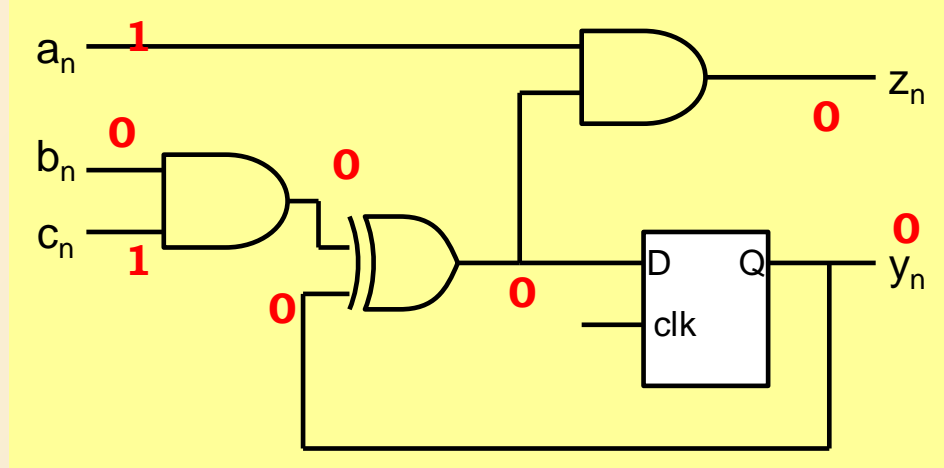


Example

 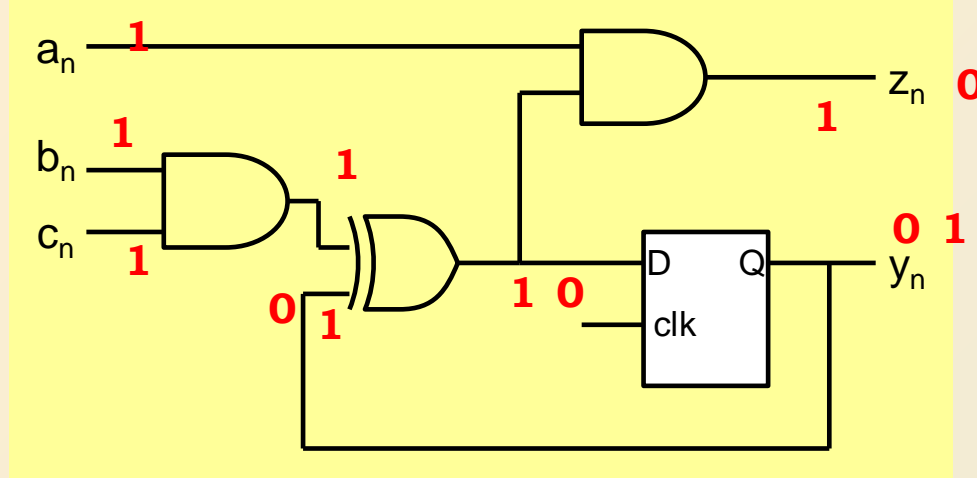



Problem with Latch

 

 Circuits are designed with the idea there would be single change in output or memory state in single clock cycle.





Edge Triggered Latch or Flip-flop


 
 


Positive edge triggered flipflop

  
Negative Edge Triggered Latch or Flip-flop




Master-Slave D Flip-flop

  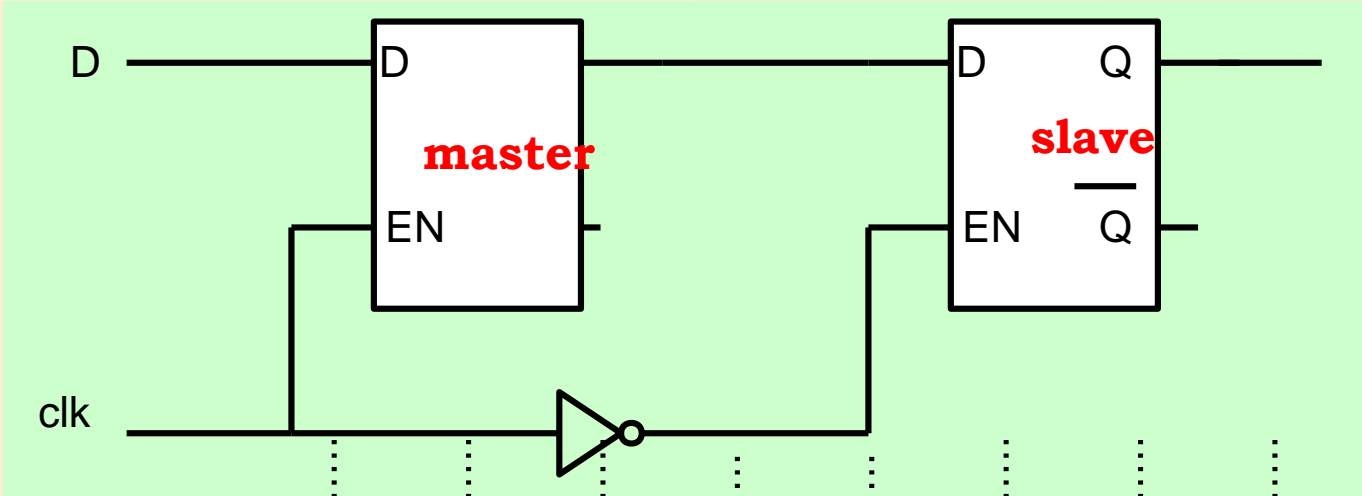

Positive edge triggered Flip-flop

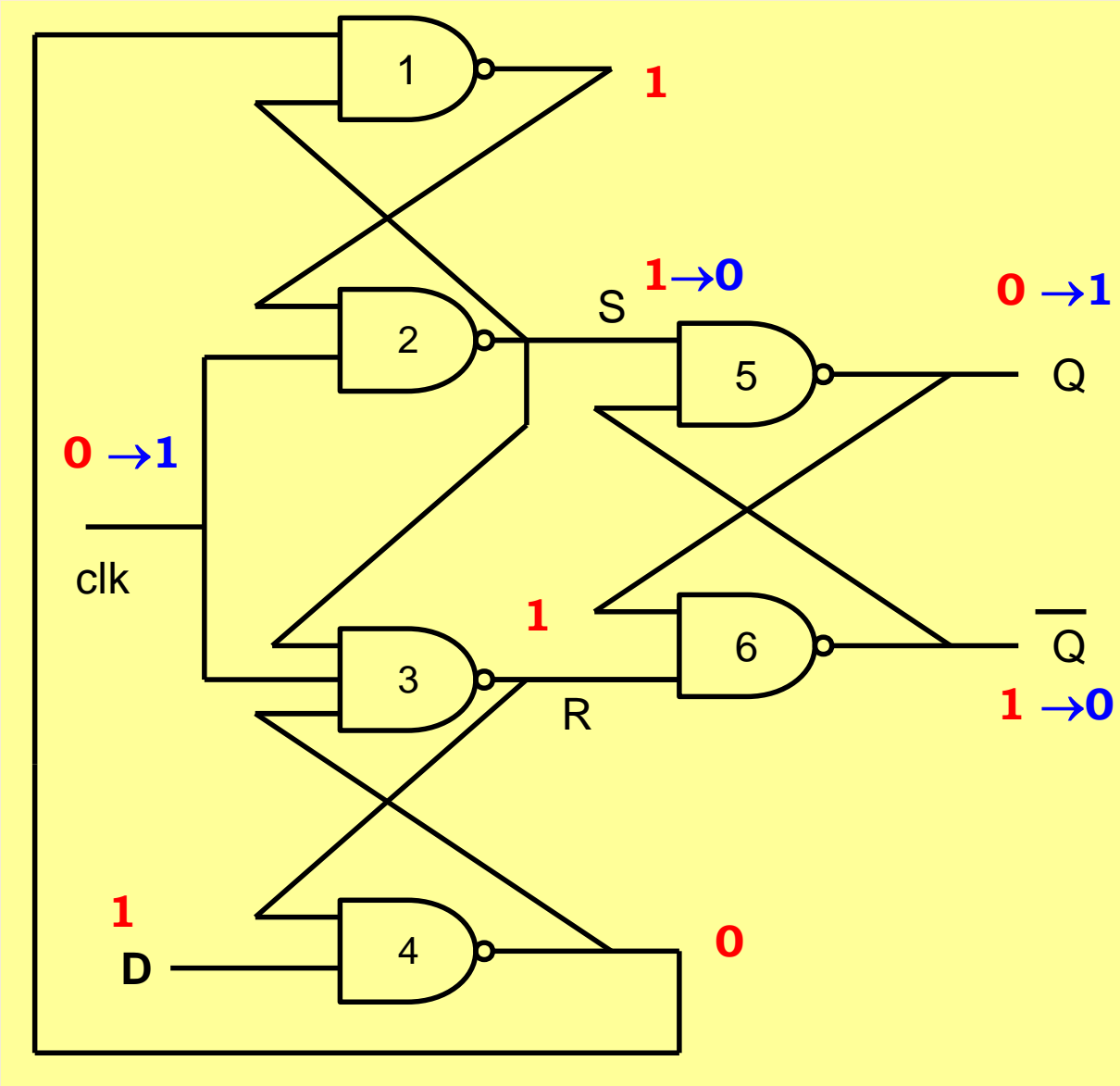


Positive edge triggered Flip-flop

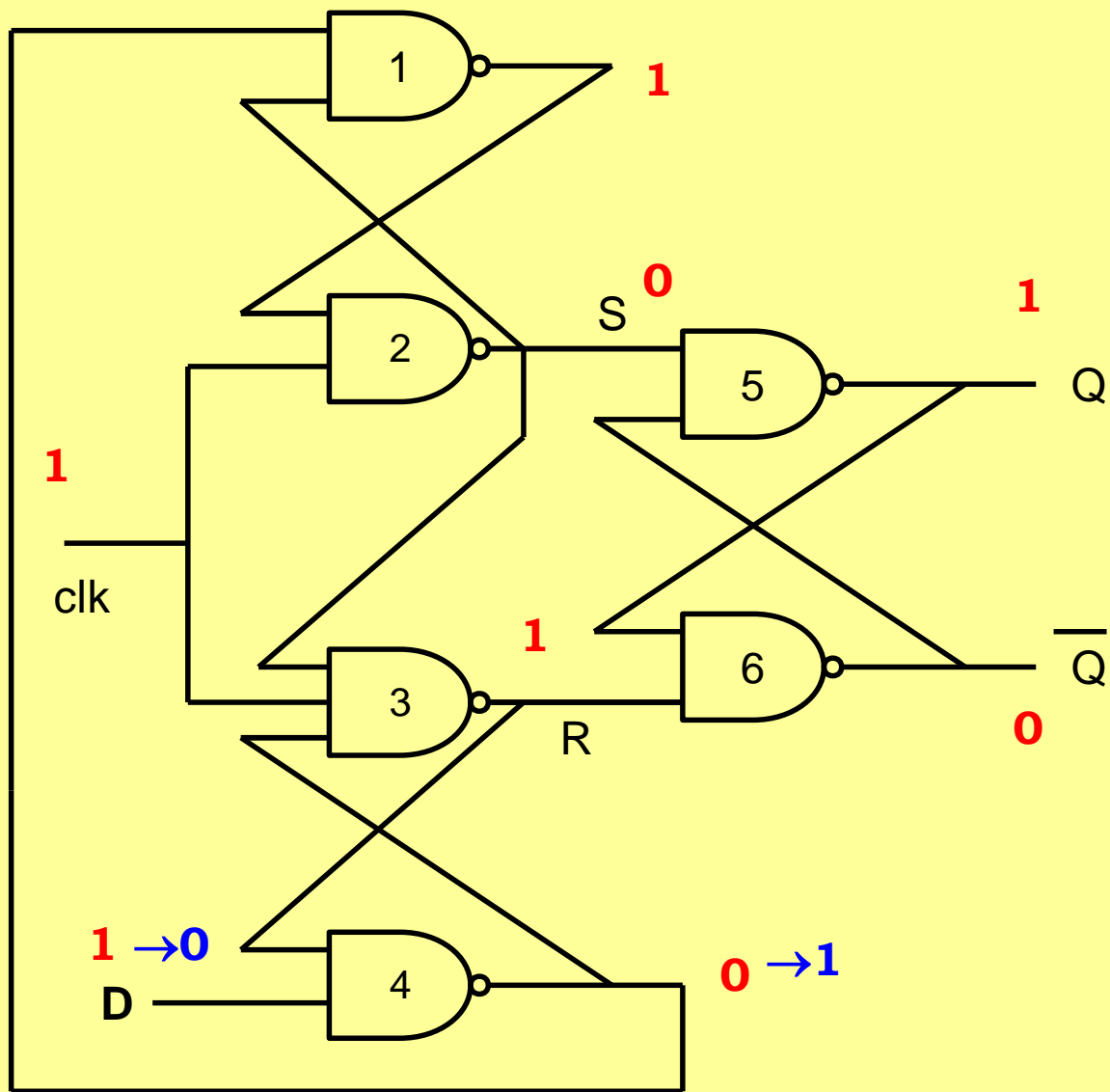


A change in input has no effect if it occurs after the clock edge

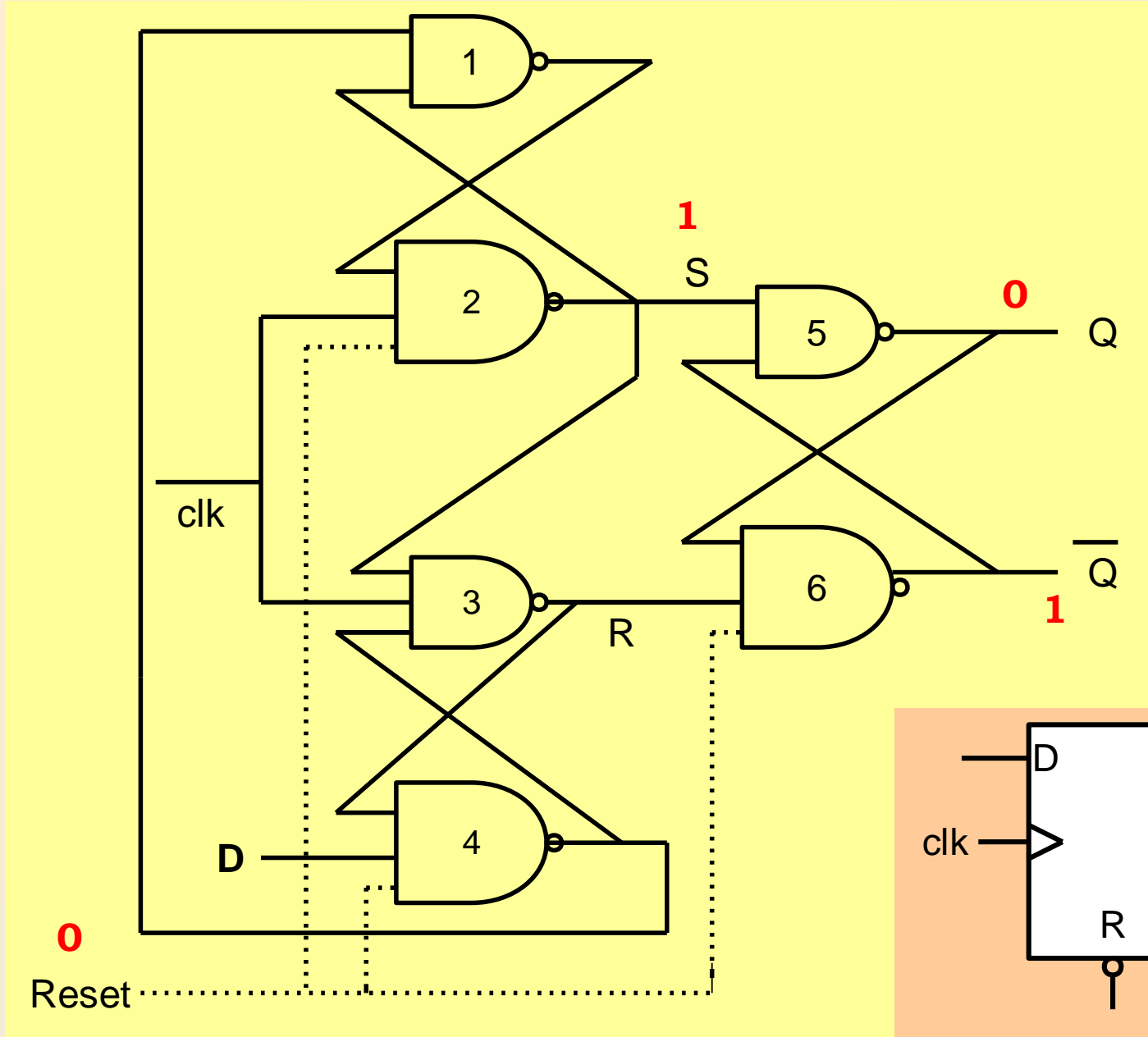Positive edge Triggered Flip-flop with Asynchronous Reset



Characteristic table

 
Given a input and the present state of the flip-flop, what is the next state of the flip-flop



Inputs (D)	Q(t+1)
0	0
1	1

$$Q(t + 1) = D$$

JK Flip-flop

 


Inputs J	K	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	$\overline{Q(t)}$

$$Q(t + 1) = \overline{Q(t)}.J + Q(t).\overline{K}$$

→Characteristic equation

Toggle or T Flip-flop

 


Inputs (T)	Q(t+1)
0	Q(t)
1	$\overline{Q(t)}$

$$Q(t+1) = \overline{Q(t)}.T + Q(t).\overline{T}$$

Excitation Table What inputs are required to effect a particular state change


Inputs		
Q(t)	Q(t+1)	T
0	0	0
0	1	1
1	0	1
1	1	0

Excitation Table

 

J	K	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	$\overline{Q(t)}$


Inputs		
Q(t)	Q(t+1)	J K
0	0	0 X
0	1	1 X
1	0	X 1
1	1	X 0

 

D	Q(t+1)
0	0
1	1

Inputs		
Q(t)	Q(t+1)	D
0	0	0
0	1	1
1	0	0
1	1	1

Convert a D FF to JK FF

 

J	K	Q(t+1)	D
0	0	Q(t)	Q(t)
0	1	0	0
1	0	1	1
1	1	$\overline{Q(t)}$	$\overline{Q(t)}$

Q \ JK	00	01	11	10
0	0	0	1	1
1	1	0	0	1

$$D = \overline{Q}.J + Q.\overline{K}$$

